

Massachusetts Institute of Technology
Department of Aeronautics and Astronautics

16.682 – Special Subjects in Aeronautics and Astronautics
“Prototyping Avionics”

Homework #2

Out: Mon Feb 27, 2006


Due: Wed Mar 8, 2006

Topics:

- Power supplies
- Transistors

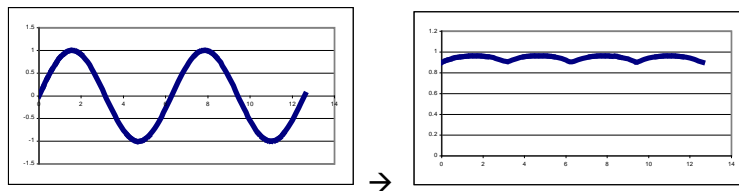
Problem 1 – Transformers and Bridges

In class we saw the use of a *full-wave bridge rectifier* to help convert an AC signal to a DC signal (with some ripple):



There are other types of rectifiers (half-wave, for example) and other ways to implement a full-wave rectifier. Lets take a quick look at these:

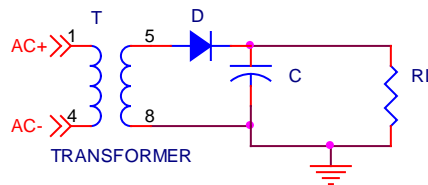
1) A half-wave rectifier looks like this:



Explain using a diagram that compares the input voltage (AC+/-) and the output voltage (V across R_L) why it is a *half wave*. The following steps could be useful:

- Assume the capacitor C is not there:
 - how does the current flow across R_L when the AC is on the positive side?
 - how does the current flow across R_L when the AC is on the negative side?
- Add the capacitor and show the approximate signal

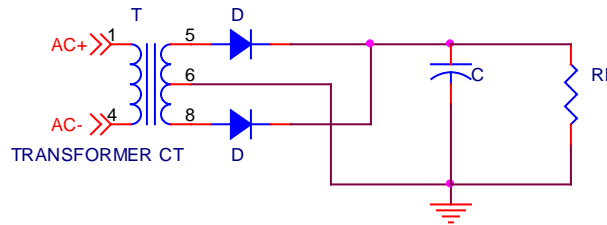2) Another way to implement a full wave rectifier is as follows (note it is *not* a *bridge*):



This is a great way to understand the concept that voltages are relative and at the same time how transformers can help us:

- Since pin 6 is defined as ground, what is the AC polarity of pins 5 & 8?
How about the DC polarity (after the diodes) of pins 5 & 8?
- Ignoring the capacitor, show how the current flows when the AC voltage is positive and negative
- Draw a picture of the output voltage before the capacitor, and compare it to the input voltage
- What happens when you account for the capacitor?
- Extra credit.** what is the main difference in the output voltage between a *bridge* rectifier (from lecture) and a *center-tap* rectifier?

Problem 2 – Regulators

After reducing the voltage with a transformer and rectifying any AC signals, you practically always want to use a regulator. Lets make sure you understand the benefits and caveats of both linear and switching regulators.

- Lets start with a linear regulator, and use it in two cases:
 - Assume that your rectifier output voltage is 12V and your load operates at 5V and utilizes:
 - 10mA of current
 - 1A of current
 What is the absolute/total wasted power in the regulator?
 What is the efficiency for each case?
 Does it make sense for a *linear* regulator?
 - Now assume the rectifier output voltage is 6V, and the current is 1A.
 What is the wasted power?
 What is the efficiency?
 - In which of these cases would you use a linear regulator? Why?

2) When you use a center-tap rectifier, or if you use batteries as your power-source, it is hard to get negative voltages. You could change your circuit to use a full-bridge and change your transformer, or could try to put “center taps” on batteries in series, but those are all ugly solutions. It would be nice to use a switching regulator!

- a) Go online and find a switching regulator that can invert a voltage (recommended sites include: <http://www.digikey.com> or <http://www.maxim-ic.com>. I don't necessarily want to promote specific brands, but these have the following benefits:
- Typing "voltage regulator" in the Digikey search box gives you a great list of results with many ways to filter out the "specifications" you want
 - Maxim provides very good datasheets with "typical application circuits" which show you how to implement a switching regulator, including all part numbers!


There are many others out there, but these give you good information.

- b) Once you find the specific regulator, get the datasheet and find:
- Maximum input voltage
 - Efficiency (maybe as a function of current?)
 - Maximum power (W)
- c) Copy a "typical application circuit" and label all the parts in it, with short explanations of the purpose of each part.

This problem intends to show you two things: understand the use of regulators, and realize that you don't have to know how to design a switching one, all you need to do is understand how they work and go find one that already exists!

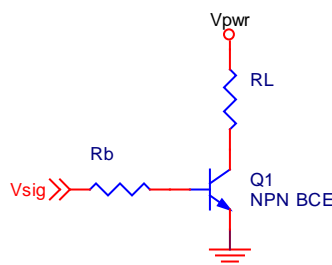Problem 3 – Transistors: NPN & PNP

For this problem we'll stick to the basic use of a transistor to amplify current of a digital circuit to drive a large load (such as a solenoid valve, a relay, etc). The circuit we presented in class is:



Reminder of something we covered in lecture too quickly: the voltage drop across a transistor (between the base and the emitter) is 0.6V in general, like in a diode.

Lets make sure you understand this circuit:

- a) If you assume that V_{sig} comes from a digital micro-controller and is either 0V or 5V; that the load requires 250mA; and that the amplification of the transistor is $h=100$, then:
 What should R_B be?
 What happens if you make R_B larger?
 What happens if you make R_B smaller?
- b) If you know that V_{sig} is 5V and can provide a maximum of 20mA, and that the transistor has $h=100$ then:
 i) What is the maximum current through the load?
 II) What is the minimum value R_B can be?


Problem 4 – Transistors: MOSFETs

1) First, let's understand the difference between N-channel and P-channel MOSFETs – it is very similar to the difference between NPN and PNP transistors. In class we saw that the current flow from *drain* to the *source* of an N-channel MOSFET is a (non-linear) function of the voltage across the *gate* (+) and the *source*(-). A P-channel MOSFET is the complement of the N-channel:

- The current flow from the *source* to the *drain* is a function of the voltage across the *source*(+) and the *gate*(-).

Draw the behavior of this current (show how current flows from one point to another) in a symbol of a P-MOSFET and draw the curve as a function of V_{gs} to I_{ds} .

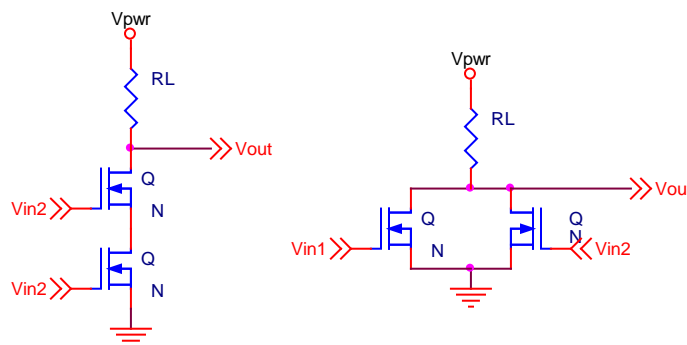2) In class we introduced MOSFETs to design digital circuits, but we only talked about the output as being “current on/off”. A real circuit requires that all nodes be fully defined and loops are closed. Therefore, let's look at slightly modified versions of the networks that were introduced in class:



In these cases we no longer have “floating” voltages, but instead all nodes are tied to a voltage, like it should be.

Keeping in mind that when the voltage between the *gate* and the *source* is positive, MOSFETs transmit current across the *drain* and the *source*, fill out the truth tables (2 total) for each of the circuits.

What are the logic functions implemented by these circuits?

3) **Extra Credit:** Try to use P-channel MOSFETs to implement the opposite logic.

That implementation is the “complimentary” circuit, and a combination of both circuits is what is ultimately used in CMOS technology.