

AERO | ASTRO



16.682 - Prototyping Avionics Spring 2006

LECTURE 5

February 22, 2006

DEPARTMENT OF AERONAUTICS AND ASTRONAUTICS

Alvar Saenz-Otero

Outline

- **Power Regulation**
 - Transformers
 - Rectifiers
 - Linear Regulators
 - Switching Regulators
- **How much power?**


Transformers

- **Exchange voltage for current to reduce potential difference (voltage) across two points**
 - The difference in number of turns between the two windings determines the ratio of voltage input to voltage output

$$\frac{v_1}{v_2} = \frac{N_1}{N_2}$$

$$\frac{i_1}{i_2} = -\frac{N_2}{N_1}$$

$$\frac{v_1}{v_2} = -\frac{i_2}{i_1}$$


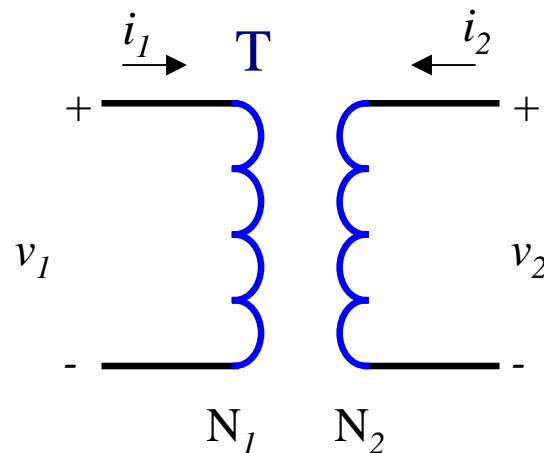


- **Note: no *conductive* element between v_1 and v_2 !**

Transformers: Multiple Types


- **Single-tap**

- One voltage output

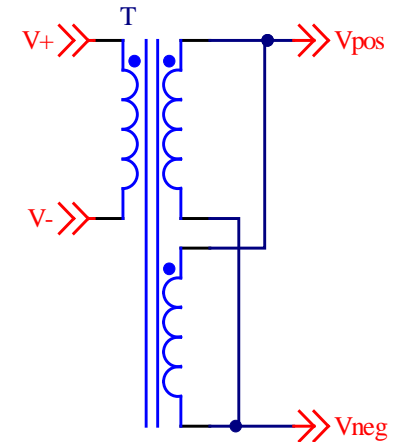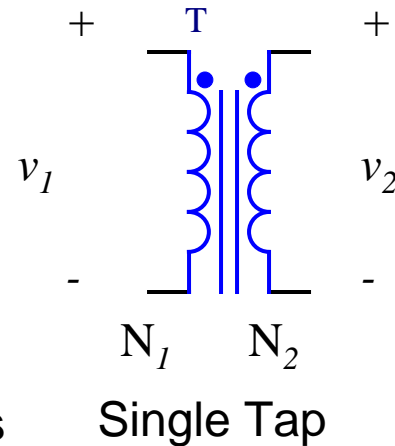


- **Multiple-taps/windings**

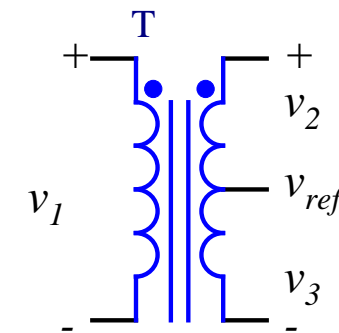- Provide multiple voltage outputs
- Multiple taps
 - Must share common point
- Multiple windings
 - Can use in series (like a tap) to get multiple voltages or in parallel to increase current output



Center Tap
configured for +V & -V

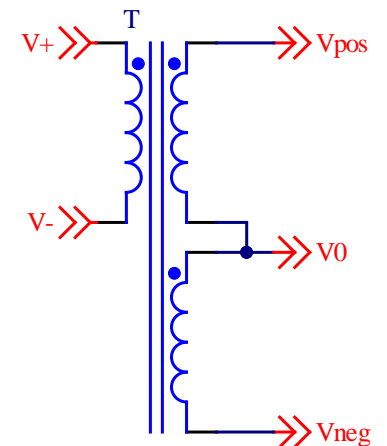


Two Windings


Rectifiers

- **DC vs AC**

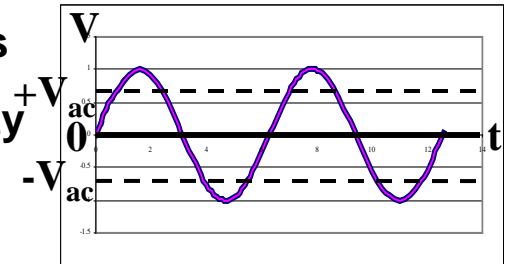
- **DC = Direct Current:** used in most electronics & batteries
- **AC = Alternating Current:** used during common electricity generation (power plants, motors with rotating magnets)
 - Preferred method to transmit over long distances



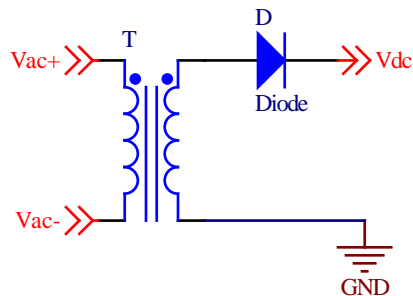- **For DC projects must convert AC to DC: use rectifiers**



Half Wave Rectifier

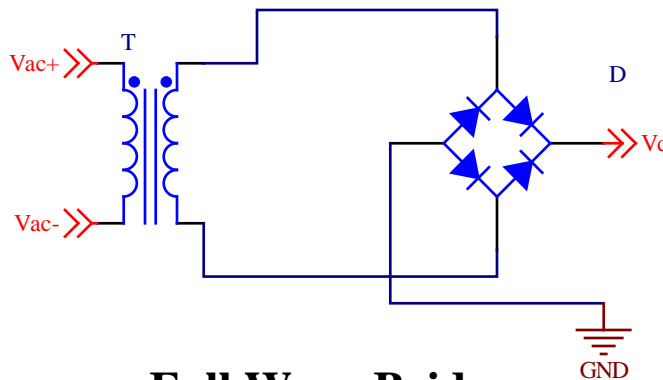

Full Wave Bridge


- **Many types:**

- **Most common: half wave and full wave**

Note: Volts AC is given in RMS value, which means the peak is at


$$V_{pp} = \frac{1}{0.707} V_{ac}$$

AC Voltage Plot

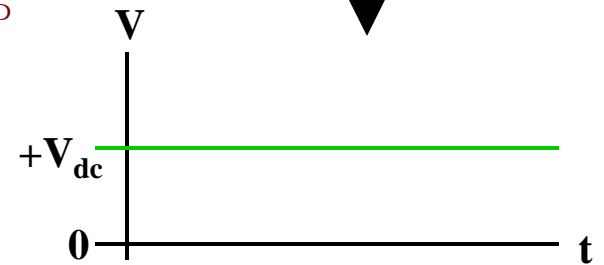


Full Wave Rectifier

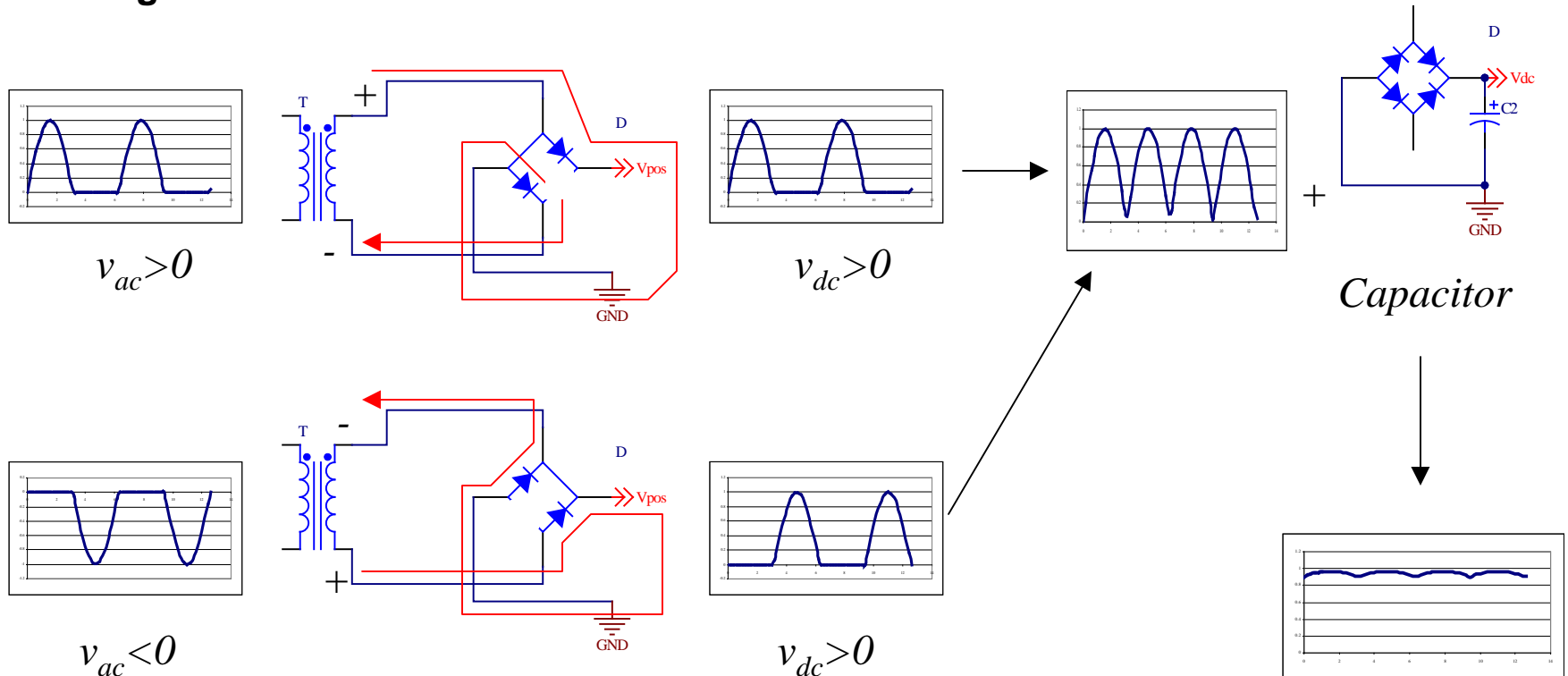- A full-wave bridge rectifier effectively provides $\text{abs}(V_{ac})$ at the output
 - A capacitor “flattens” the sinusoidal AC signal for a relatively flat DC output
 - The output will always have some *ripple*, must use a regulator to fully flatten the signal




Linear Regulators

- Regulate an input voltage to:
 - Reduce voltage to exact needs
 - Provide constant output
 - No ripple
 - Regardless of load (even changing load)
- Simplest design of all regulators
 - Only needs capacitors as external components, no high-frequency elements
- Input voltage (abs) **MUST** be higher than output voltage (abs)
 - Linear regulators cannot increase or invert voltage
- Power lost in regulator is linear WRT current pull and voltage drop ($V_{in} - V_{out}$)
 - Useful for small current and/or small voltage drop
- Efficiency is linear WRT the voltage drop ($V_{in} - V_{out}$)
 - Most efficient with small voltage drop...

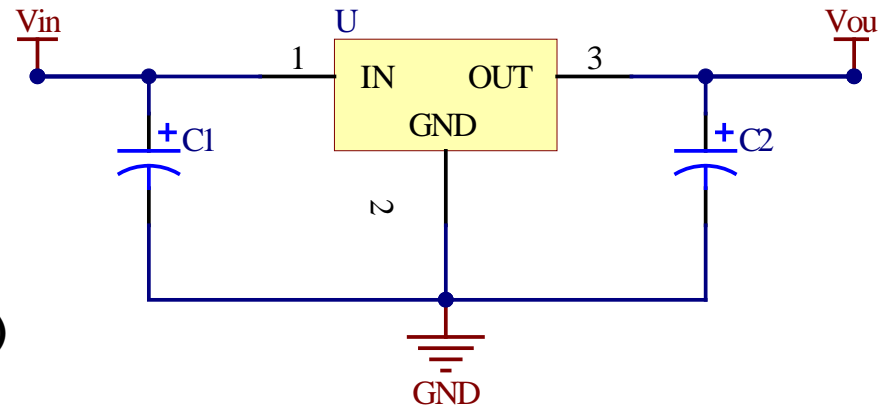

Linear Regulator Model

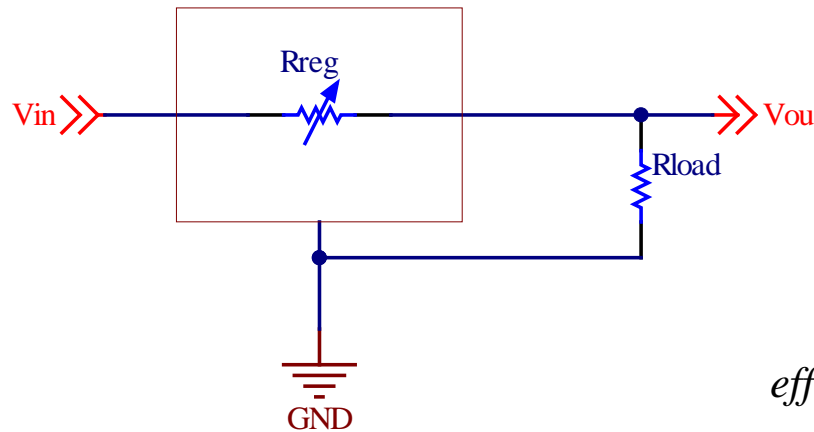- The simplest model of a linear regulator is a *variable resistor*:



$$i_{out} = \frac{V_{out}}{R_{load}}$$

$$i_{in} = i_{out}$$


$$P_{reg} = i_{out} (v_{in} - v_{out})$$

$$eff = \frac{P_{out}}{P_{reg} + P_{out}} = \frac{i_{out} v_{out}}{i_{out} (v_{in} - v_{out}) + i_{out} v_{out}} = \frac{v_{out}}{v_{in}}$$

- The effective resistance of the circuit, R_{load} , determines the necessary current
 - The input current must be the same as the output current
- Example:**
 - $V_{in}=7V, V_{out}=5V, i=100mA$
 - $P_{reg} = 0.2W, P_{tot} = 0.7W, eff = 71%$ reasonable use, no heatsink
 - $V_{in}=7V, V_{out}=5V, i=1A$
 - $P_{reg}= 2W, P_{tot}= 7W, eff=71%$ **NEED heatsink to dissipate 2W!**
 - $V_{in}=20V, V_{out} =5V, i=100mA$
 - $P_{reg}= 1.5W, P_{tot} = 2W, eff=25%$ **UNreasonable use, a lot of power wasted, low efficiency!**

Switching Regulators

- Regulate an input voltage to:
 - Decrease, increase, and/or invert a voltage
 - Allow for large input/output voltage differentials
 - Can only increase or decrease voltage, not both
 - Practically get rid of ripple
- Complex design
 - Uses many external components
- Design uses an inductor to create the necessary voltage by driving current through it at high frequencies (~100-500kHz)
 - Utilizes feedback of both current (through sense resistor) and voltage (at output)
 - Output voltage has small noise at operating frequency, usually insignificant
- Usually 80-95% efficiency, dependent on current pull
 - Driving the high-frequency signal requires a minimum constant power input, even if the output is disconnected (no current)

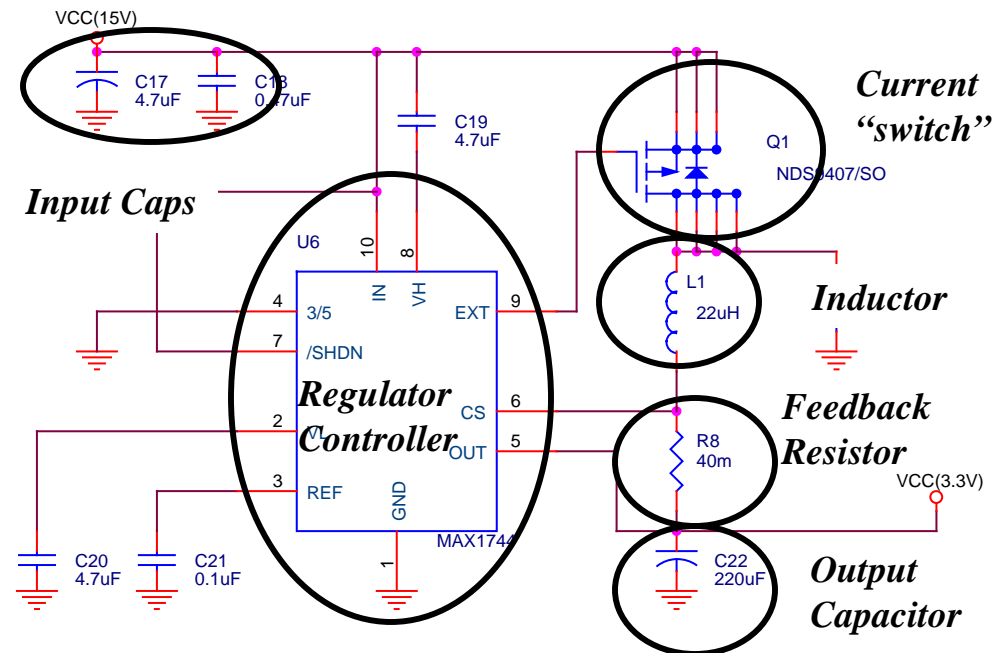

Switching Regulator Model

- **No simple model**
 - It is a feedback loop where the sensor drives the “current switch” as necessary
- **For design purposes can assume that power in equal power out, plus the efficiency factor**
 - For design one *must* know the necessary current supply for V_{in}

$$v_{in} i_{in} = P_{in} = P_{out} = v_{out} i_{out}$$

$$i_{in} = \frac{v_{out} i_{out}}{v_{in}} \cdot \frac{1}{eff}$$

- **Example: from datasheet, since the model of a switching regulator is not always the same**
 - Note different curves for different input voltages
 - Note very low efficiency for low output currents

How much power do you need?

- **Remember it is very simple:**
 - **$P = IV$, always as far as we're concerned**
 - **Power can be added**
 - **If you know the power of individual components, and are given the voltage & current for others, add the power together!**
 - **Account for regulator efficiency**
 - **Select the best type of regulator for your needs, consider both design (linear is simple) and efficiency/power dissipation (usually switching is better)**
 - **Allow for at least 20% margin**
 - **After considering regulator efficiency**