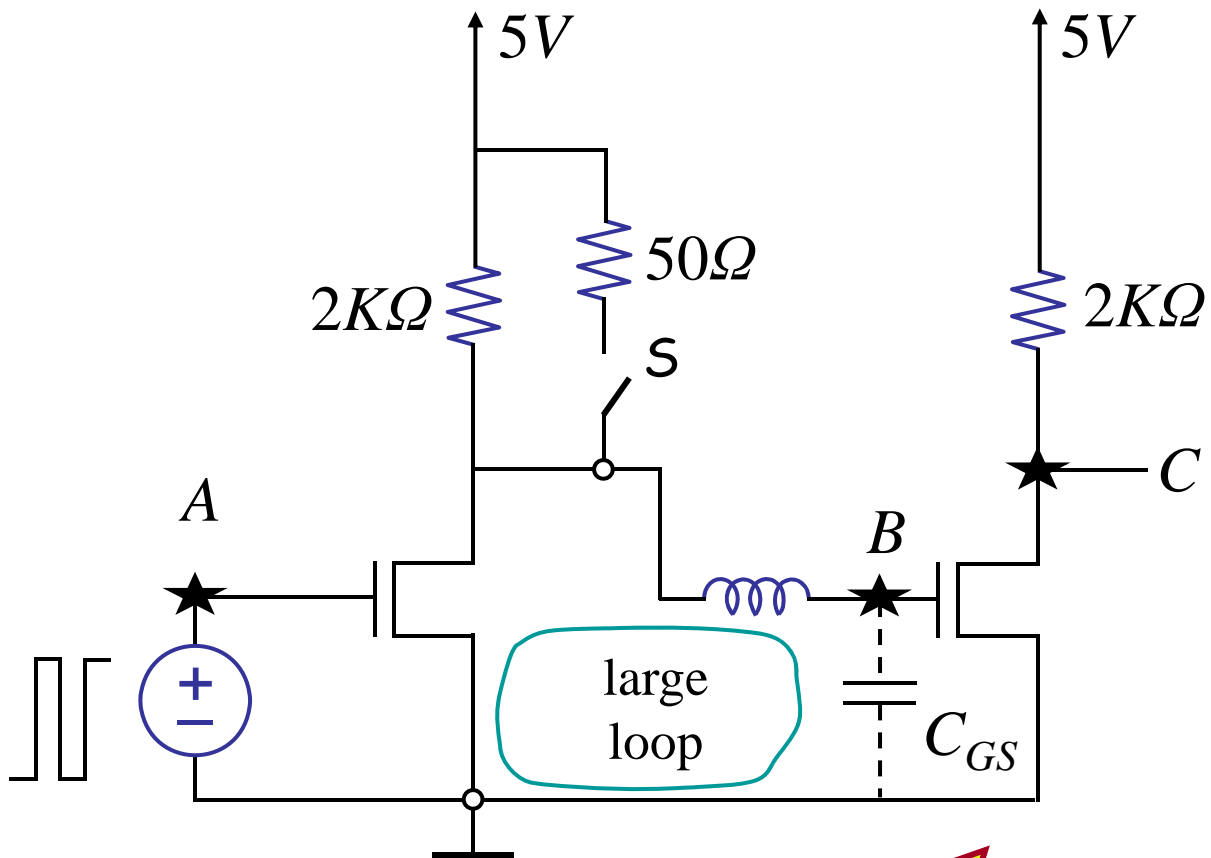


Damped Second-Order Systems

Damped Second-Order Systems




Remember this Demo


Our old friend, the inverter, driving another. The parasitic inductance of the wire and the gate-to-source capacitance of the MOSFET are shown

[Review complex algebra appendix in Agarwal & Lang for next class]


Damped Second-Order Systems

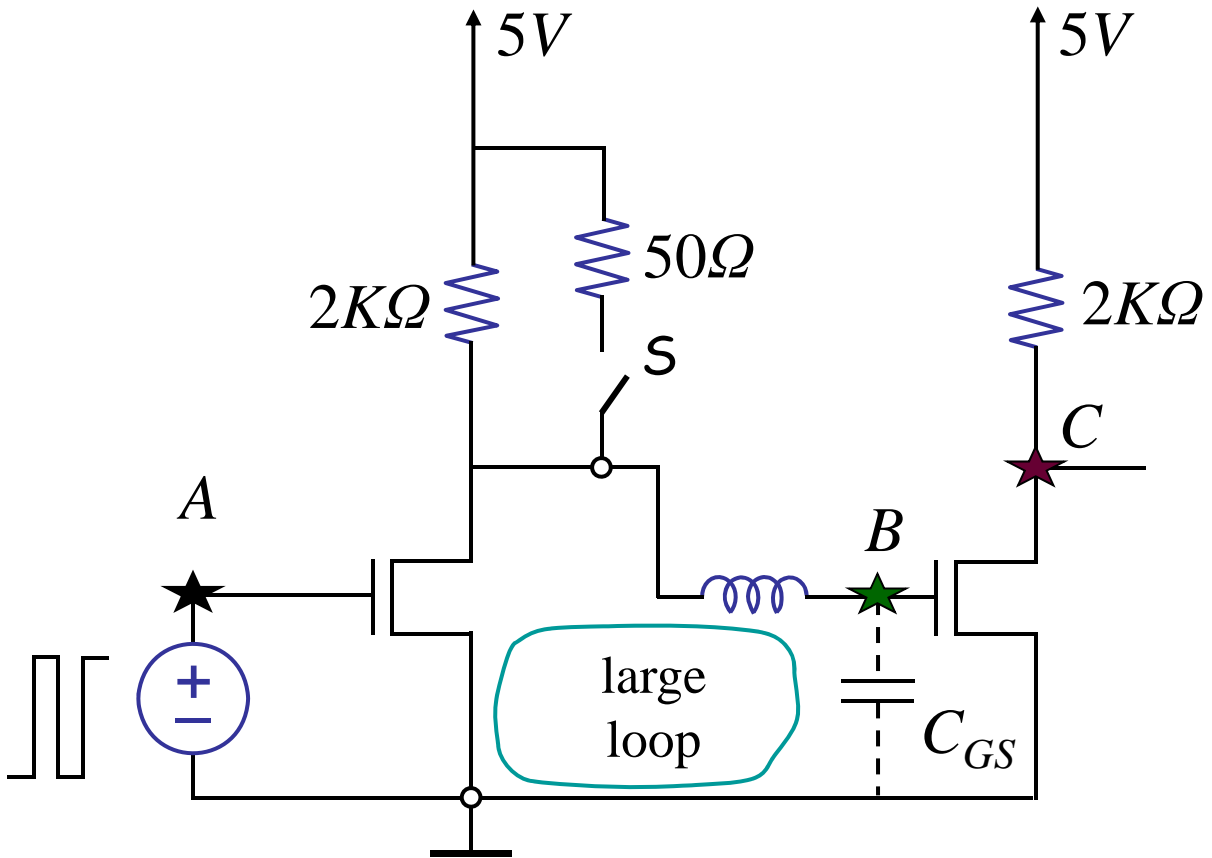

Relevant circuit:

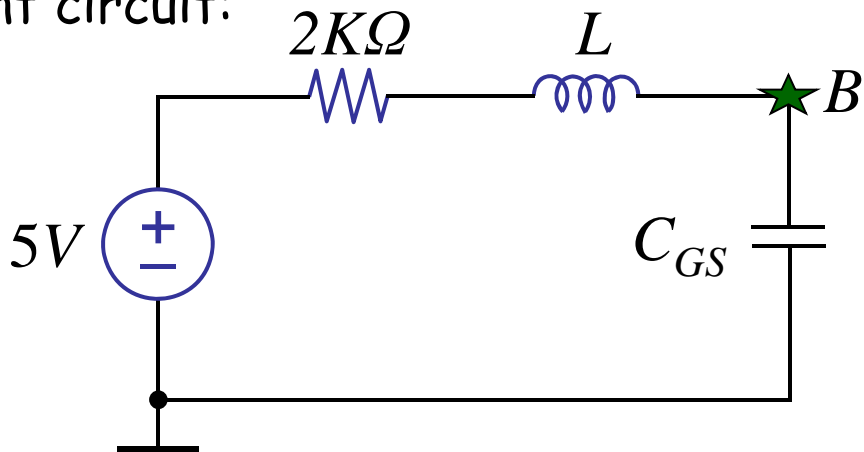


Observed Output $2k\Omega$

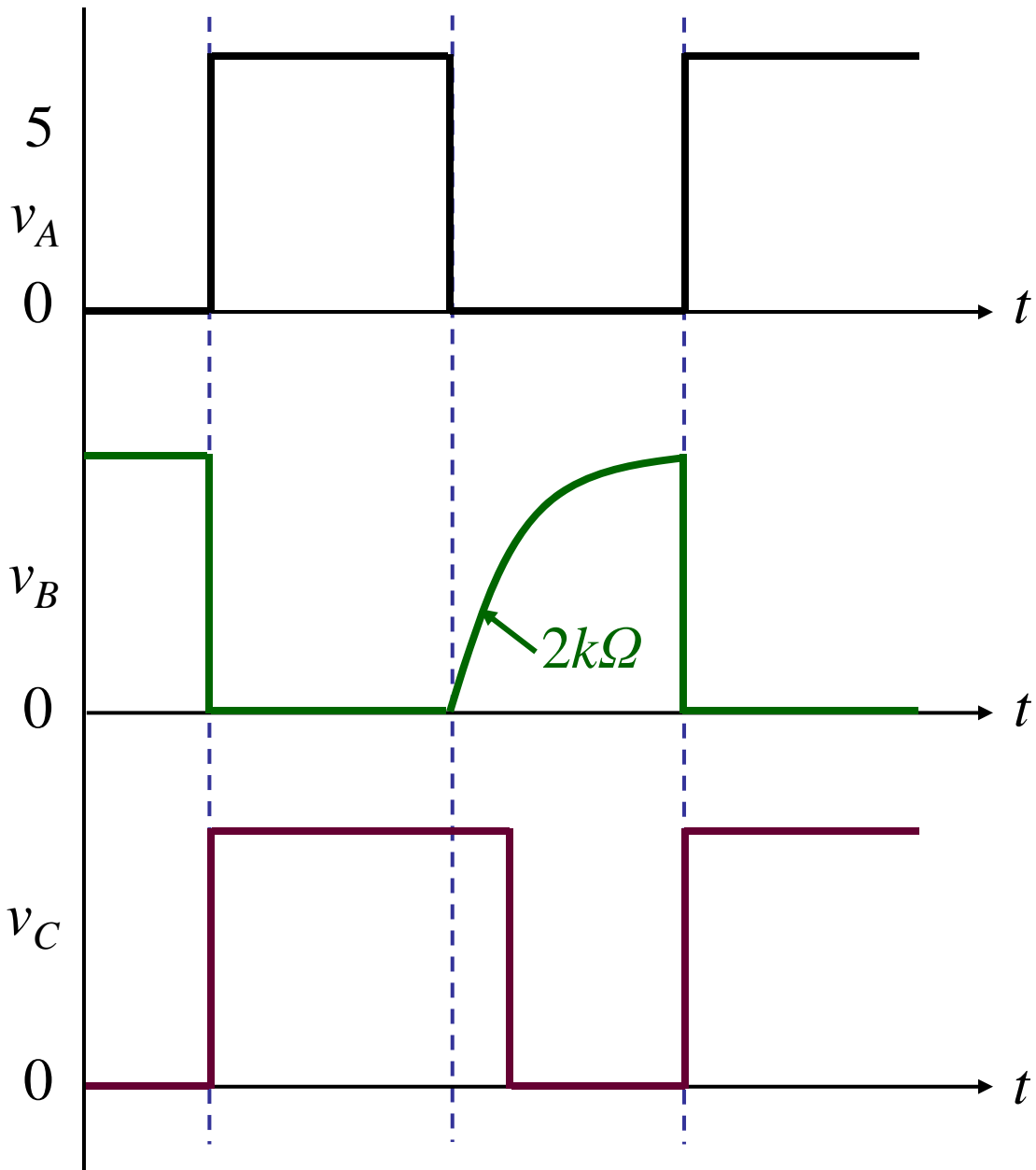


Now, let's try to speed up our inverter by closing the switch S to lower the effective resistance

Observed Output $\sim 50\Omega$

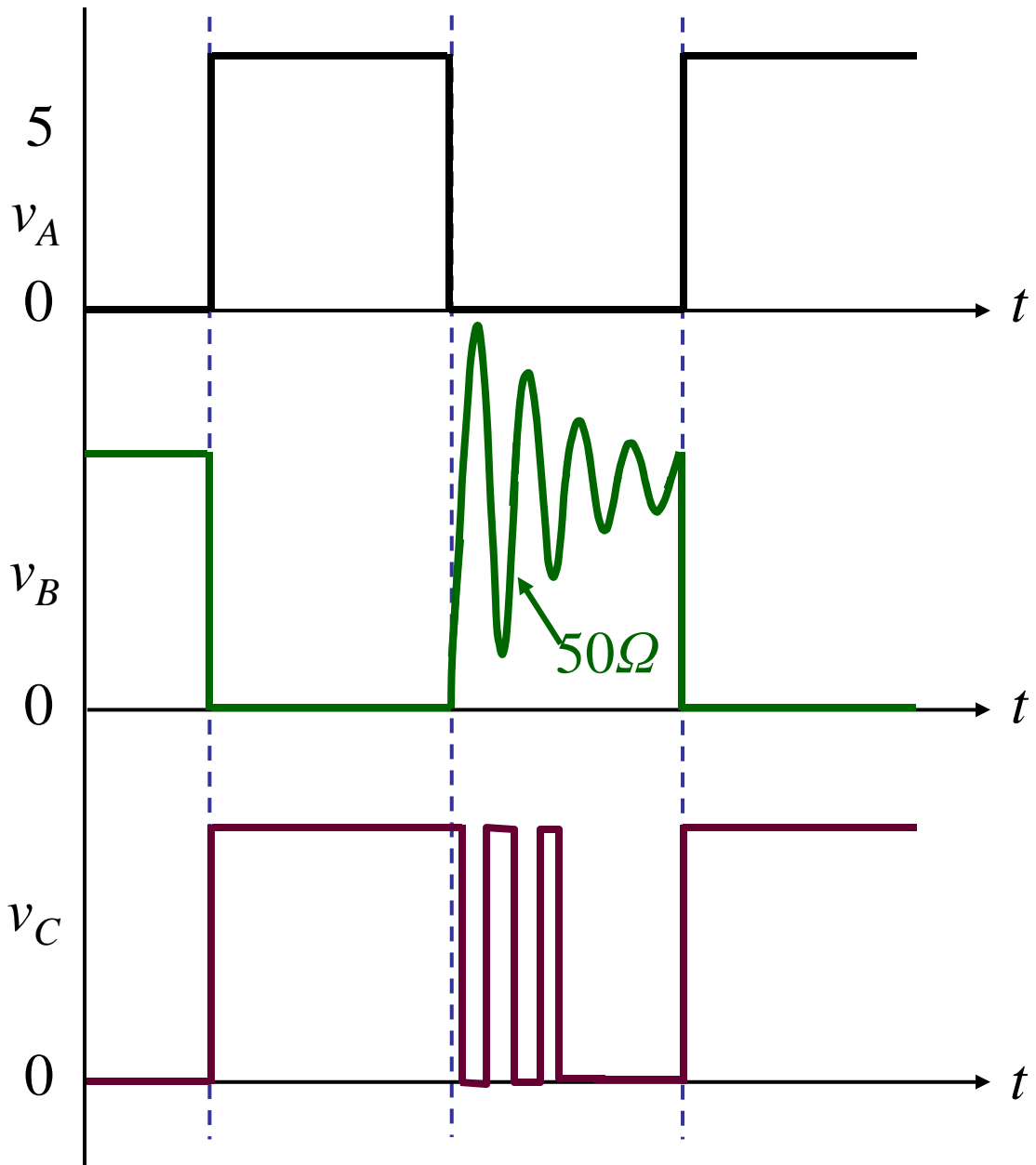

Huh!

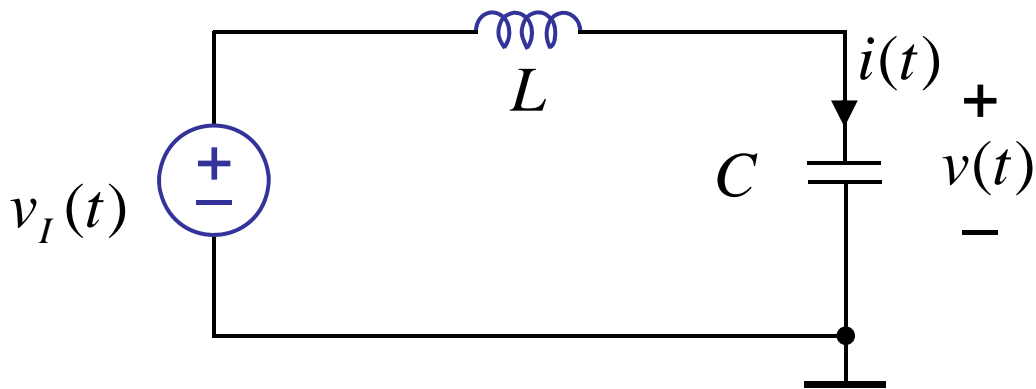In the last lecture, we started by analyzing the simpler LC circuit to build intuition




In the last lecture...

We solved

$$\frac{d^2v}{dt^2} + \frac{1}{LC}v = \frac{1}{LC}v_I$$

For input

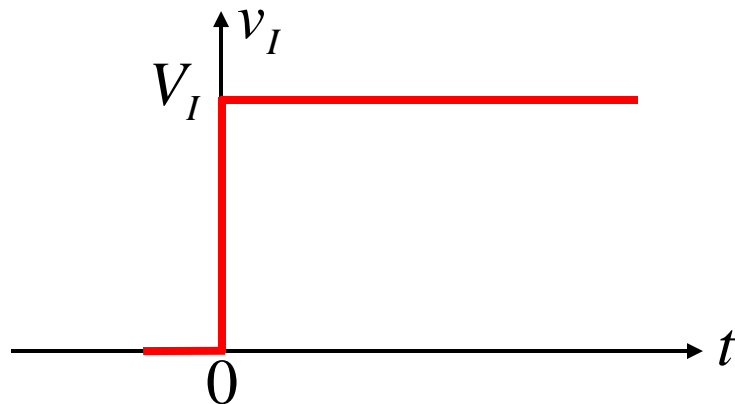

And for initial conditions

$$v(0) = 0 \quad i(0) = 0 \quad [\text{ZSR}]$$



In the last lecture...

Total solution



$$v(t) = V_I - V_I \cos \omega_o t$$

where

$$\omega_o = \frac{1}{\sqrt{LC}}$$

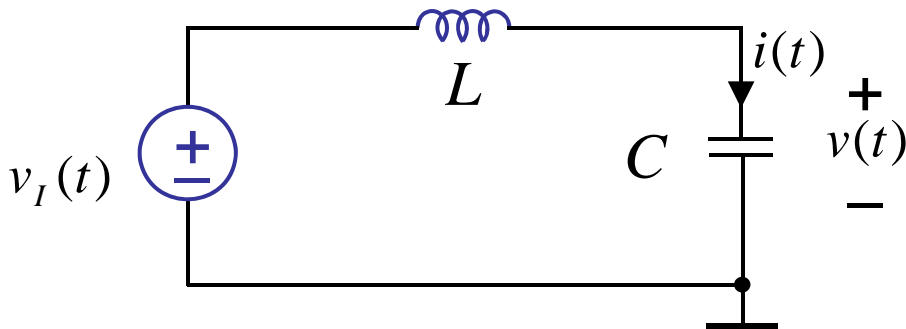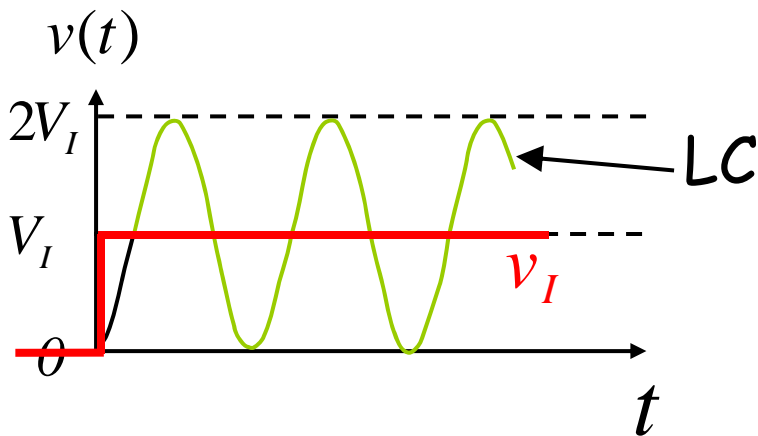

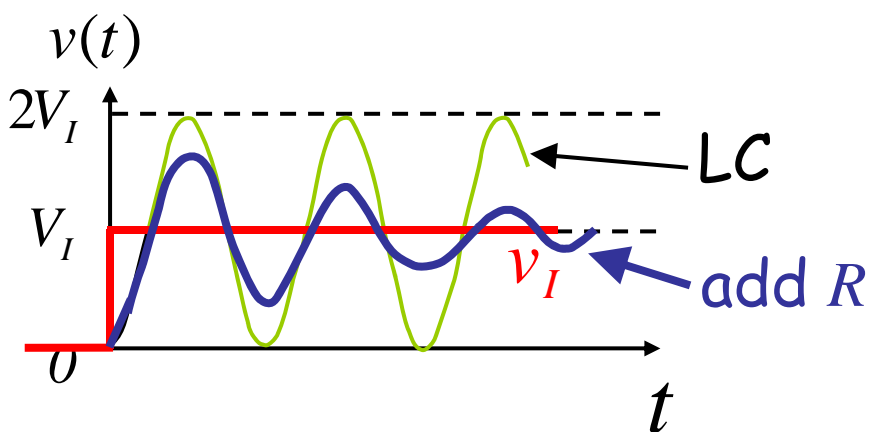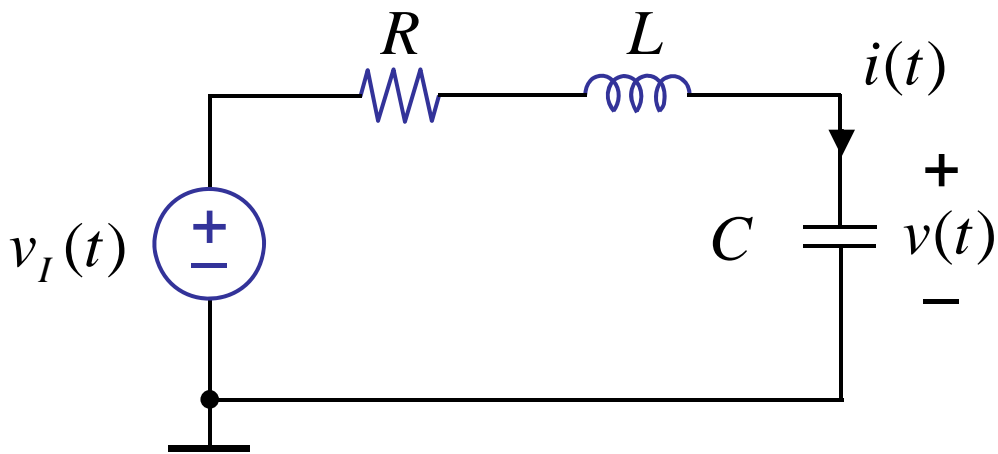
Today, we will close the loop on our observations in the demo by analyzing the RLC circuit



Damped sinusoids with R - remember demo!

See A&L Section 13.6

Let's analyze the RLC network

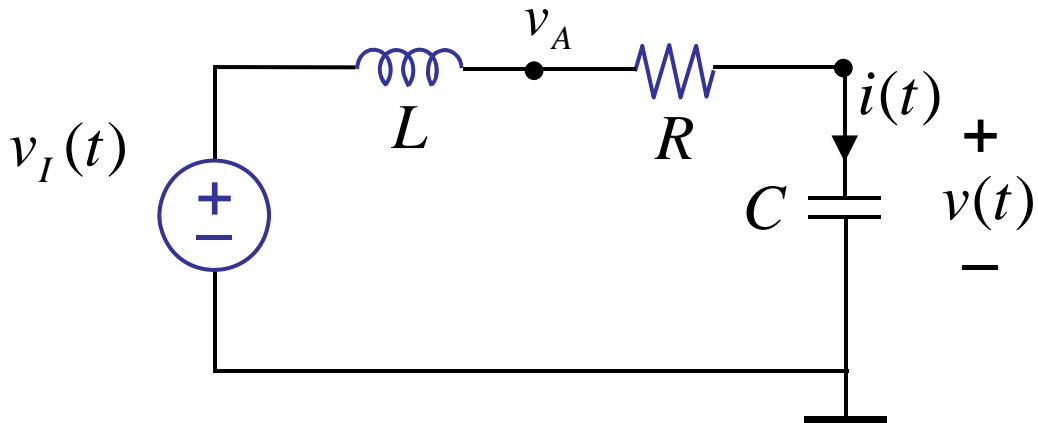

Node method:

$$v_A : \quad \frac{1}{L} \int_{-\infty}^t (v_I - v_A) dt = \frac{v_A - v}{R}$$

$$v : \quad \frac{v_A - v}{R} = C \frac{dv}{dt}$$

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

Recall
element rules

L:

$$v_L = L \frac{di}{dt}$$


$$\frac{1}{L} \int_{-\infty}^t v_L dt = i$$

C:

$$i_C = C \frac{dv_C}{dt}$$

v, i state variables

Let's analyze the RLC network

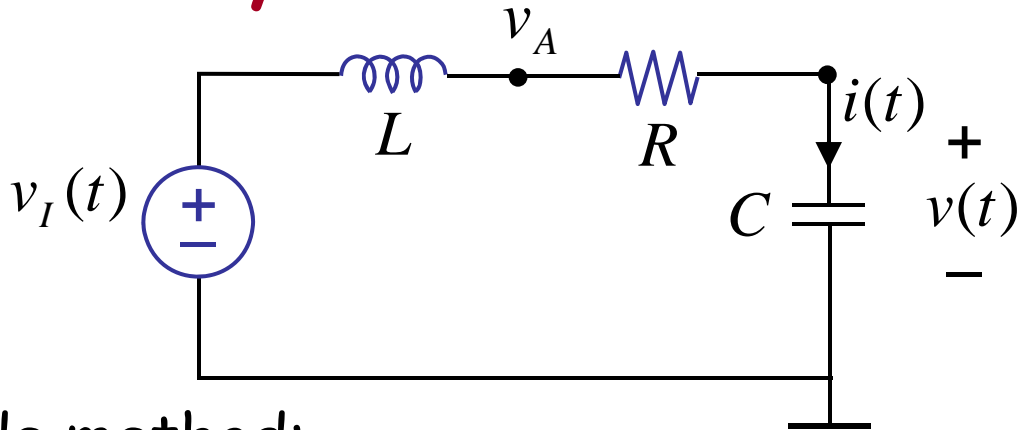

Node method:

$$v_A : \quad \frac{1}{L} \int_{-\infty}^t (v_I - v_A) dt = \frac{v_A - v}{R}$$

$$v : \quad \frac{v_A - v}{R} = C \frac{dv}{dt}$$

$$\frac{1}{L} (v_I - v_A) = C \frac{d^2 v}{dt^2}$$

$$\frac{1}{LC} (v_I - v_A) = \frac{d^2 v}{dt^2}$$

$$v_A = RC \frac{dv}{dt} + v$$

$$\frac{1}{LC} \left(v_I - RC \frac{dv}{dt} - v \right) = \frac{d^2 v}{dt^2}$$

$$\frac{d^2 v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

Solving

Recall, the method of homogeneous and particular solutions:

- ① Find the particular solution.
- ② Find the homogeneous solution.

↓
4 steps


- ③ The total solution is the sum of the particular and homogeneous.
Use initial conditions to solve for the remaining constants.

$$v = v_P(t) + v_H(t)$$

Let's solve

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = \frac{1}{LC} v_I$$

For input

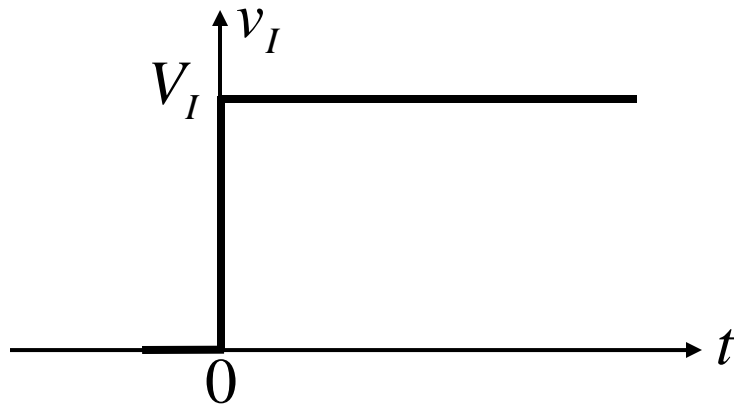

And for initial conditions

$$v(0) = 0 \quad i(0) = 0 \quad [\text{ZSR}]$$

A dashed horizontal line is drawn below the equation.

① Particular solution

$$\frac{d^2 v_P}{dt^2} + \frac{R}{L} \frac{dv_P}{dt} + \frac{1}{LC} v_P = \frac{1}{LC} V_I$$

$v_P = V_I$ is a solution.

② Homogeneous solution

Solution to
$$\frac{d^2 v_H}{dt^2} + \frac{R}{L} \frac{dv_H}{dt} + \frac{1}{LC} v_H = 0$$

Recall, v_H : solution to homogeneous equation (drive set to zero)

Four-step method:

① Assume solution of the form

$$v_H = Ae^{st} \quad , \quad A, s = ?$$

② Form the characteristic equation $f(s)$

③ Find the roots of the characteristic equation

$$s_1, s_2$$

④ General solution

$$v_H = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

② Homogeneous solution

Solution to
$$\frac{d^2 v_H}{dt^2} + \frac{R}{L} \frac{dv_H}{dt} + \frac{1}{LC} v_H = 0$$

① Assume solution of the form

$$v_H = Ae^{st} \quad , \quad A, s = ?$$

so,
$$\cancel{A} s^2 \cancel{e^{st}} + \frac{R}{L} \cancel{A} \cancel{e^{st}} + \frac{1}{LC} \cancel{A} \cancel{e^{st}} = 0$$

②

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

characteristic equation

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

$$\omega_o = \sqrt{\frac{1}{LC}}$$

$$\alpha = \frac{R}{2L}$$

③ Roots $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_o^2}$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_o^2}$$

④ General solution

$$v_H = A_1 e^{\left(-\alpha + \sqrt{\alpha^2 - \omega_o^2}\right)t} + A_2 e^{\left(-\alpha - \sqrt{\alpha^2 - \omega_o^2}\right)t}$$

③ Total solution

$$v(t) = v_p(t) + v_H(t)$$

$$v(t) = V_I + A_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_o^2})t} + A_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_o^2})t}$$

Find unknowns from initial conditions.

$$v(0) = 0: \quad 0 = V_I + A_1 + A_2$$

$$i(0) = 0:$$

$$i(t) = C \frac{dv}{dt}$$

$$= CA_1 \left(-\alpha + \sqrt{\alpha^2 - \omega_o^2} \right) e^{(-\alpha + \sqrt{\alpha^2 - \omega_o^2})t} +$$
$$CA_2 \left(-\alpha - \sqrt{\alpha^2 - \omega_o^2} \right) e^{(-\alpha - \sqrt{\alpha^2 - \omega_o^2})t}$$

$$\text{so,} \quad 0 = A_1 \left(-\alpha + \sqrt{\alpha^2 - \omega_o^2} \right) + A_2 \left(-\alpha - \sqrt{\alpha^2 - \omega_o^2} \right)$$

Mathematically: solve for unknowns,
done.


Let's stare at this a while longer...

$$v(t) = V_I + A_1 e^{-\alpha t} e^{\left(\sqrt{\alpha^2 - \omega_o^2}\right)t} + A_2 e^{-\alpha t} e^{\left(-\sqrt{\alpha^2 - \omega_o^2}\right)t}$$

3 cases:

$\alpha > \omega_o$ Overdamped
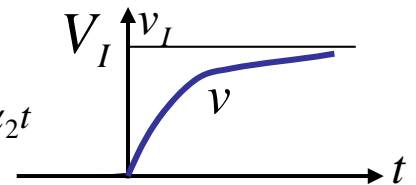
$$v(t) = V_I + A_1 e^{-\alpha_1 t} + A_2 e^{-\alpha_2 t}$$



$\alpha < \omega_o$ Underdamped

$$\begin{aligned} v(t) &= V_I + A_1 e^{-\alpha t} e^{\left(j\sqrt{\omega_o^2 - \alpha^2}\right)t} + A_2 e^{-\alpha t} e^{\left(-j\sqrt{\omega_o^2 - \alpha^2}\right)t} \\ &= V_I + A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t} \quad \left| \quad \omega_d = \sqrt{\omega_o^2 - \alpha^2} \right. \\ &= V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t \quad \left| \quad e^{j\omega_d t} = \cos \omega_d t + j \sin \omega_d t \right. \end{aligned}$$

$\alpha = \omega_o$ Critically damped
Later...

Let's stare at underdamped a while longer...

$\alpha < \omega_o$ Underdamped contd...

$$v(t) = V_I + K_1 e^{-\alpha t} \cos \omega_d t + K_2 e^{-\alpha t} \sin \omega_d t$$

$$v(0) = 0: K_1 = -V_I$$

$$\begin{aligned} i(0) = 0: i(t) &= C \frac{dv}{dt} \\ &= -CK_1 \alpha e^{-\alpha t} \cos \omega_d t - CK_2 \omega_d e^{-\alpha t} \sin \omega_d t \\ &\quad - CK_1 \alpha e^{-\alpha t} \sin \omega_d t + CK_2 \omega_d e^{-\alpha t} \cos \omega_d t \end{aligned}$$

$$0 = -K_1 \alpha + K_2 \omega_d$$

$$K_2 = -\frac{V_I \alpha}{\omega_d}$$

$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

Note: For $R = 0 \implies \alpha = 0$

$$v(t) = V_I - V_I \cos \omega_o t$$

Same as LC as expected


Let's stare at underdamped a while longer...

$\alpha < \omega_0$ Underdamped contd...

$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

Remember, scaled sum of sines (of the same frequency) are also sines! -- Appendix B.7
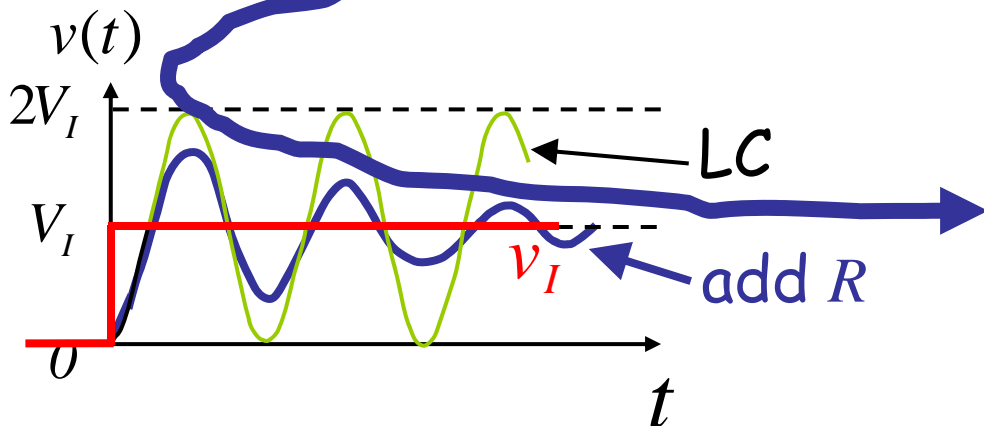
$$v(t) = V_I - V_I \frac{\omega_d}{\omega_d} e^{-\alpha t} \cos \left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d} \right)$$




$\alpha < \omega_o$ Underdamped contd...


$$v(t) = V_I - V_I e^{-\alpha t} \cos \omega_d t - V_I \frac{\alpha}{\omega_d} e^{-\alpha t} \sin \omega_d t$$

Remember, scaled sum of sines (of the same frequency) are also sines! -- Appendix B.7
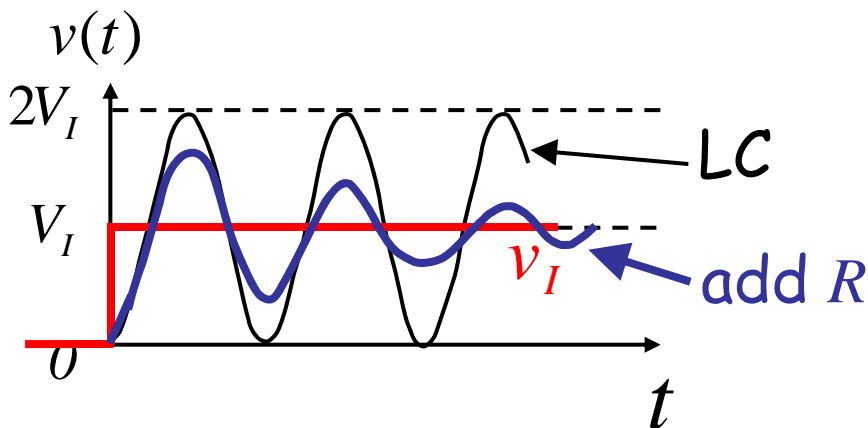
$$v(t) = V_I - V_I \frac{\omega_o}{\omega_d} e^{-\alpha t} \cos \left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d} \right)$$




$\alpha = \omega_o$ Critically damped

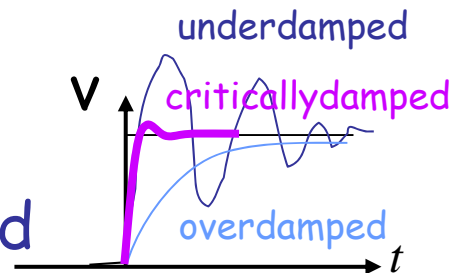

Section 13.2.3

Remember this? Closed the loop...

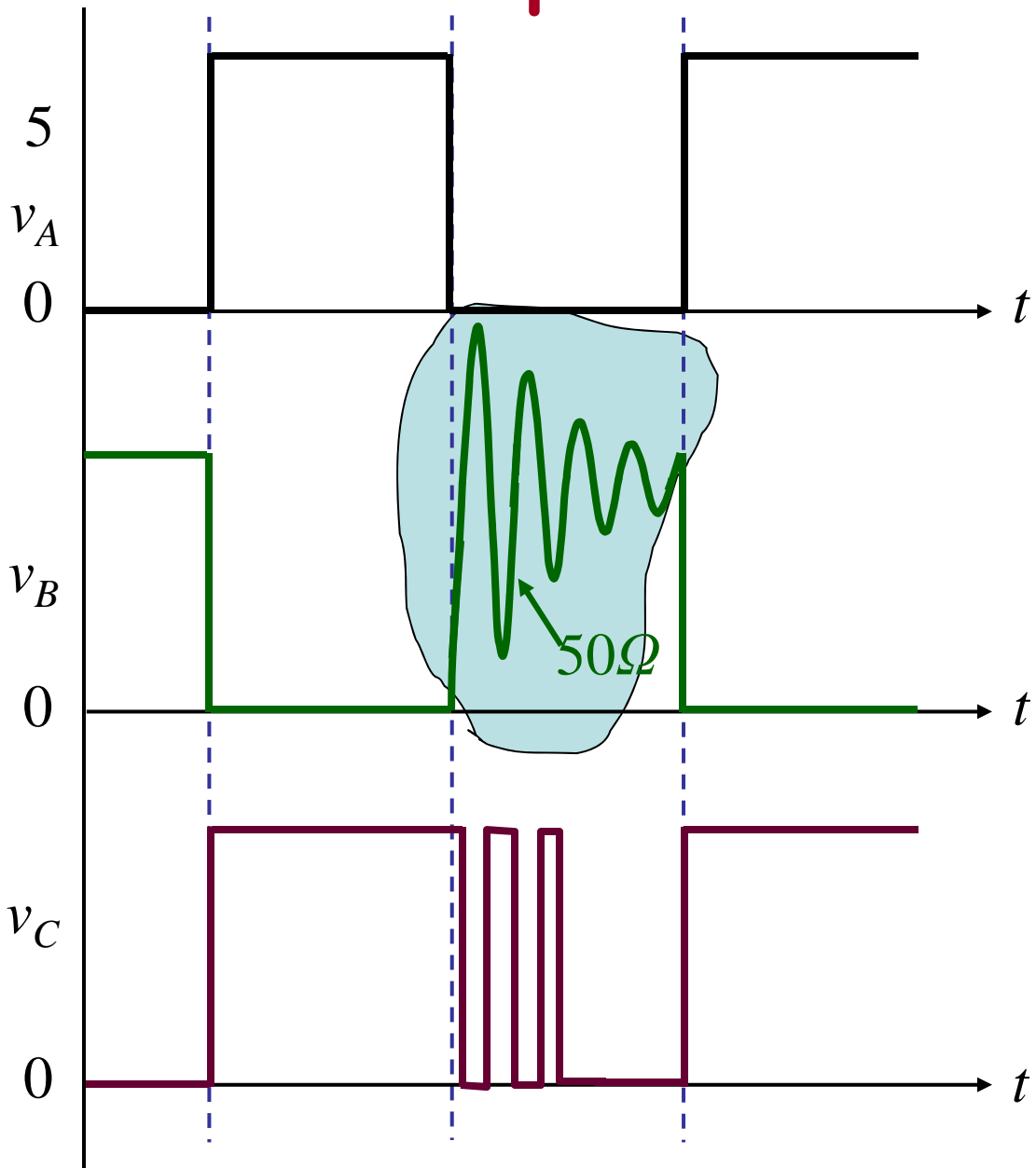


See example 12.9 on page 664 of the A&L textbook for inverter-pair analysis

Intuitive Analysis

See Sec. 12.7 of A&L textbook

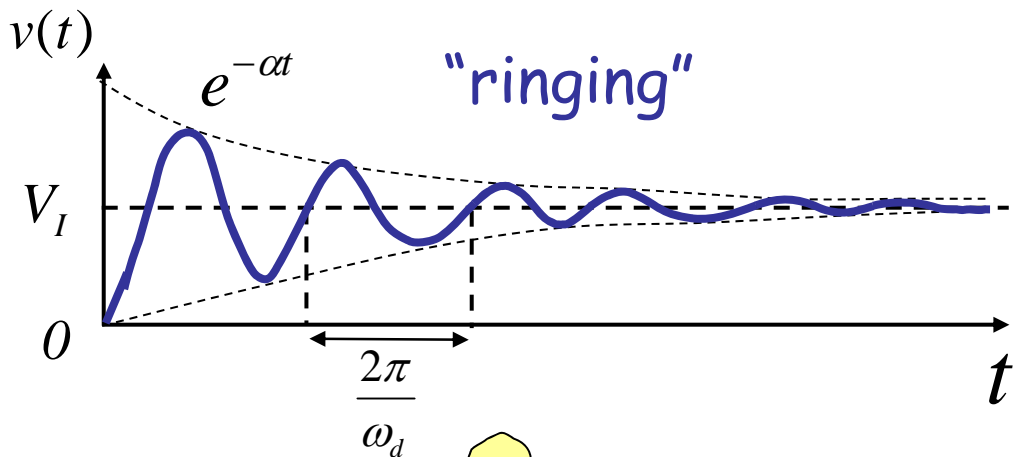Underdamped $v(t) = V_I - V_I \frac{\omega_o}{\omega_d} e^{-\alpha t} \cos\left(\omega_d t - \tan^{-1} \frac{\alpha}{\omega_d}\right)$



Characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

ω_d : Oscillation frequency $\omega_d = \sqrt{\omega_o^2 - \alpha^2}$

α : Governs rate of decay


V_I : Final value

$v(0)$: Initial value

$Q = \frac{\omega_o}{2\alpha}$: Quality factor (approximately the number of cycles of ringing)

Intuitive Analysis

See Sec. 12.7
of A&L textbook

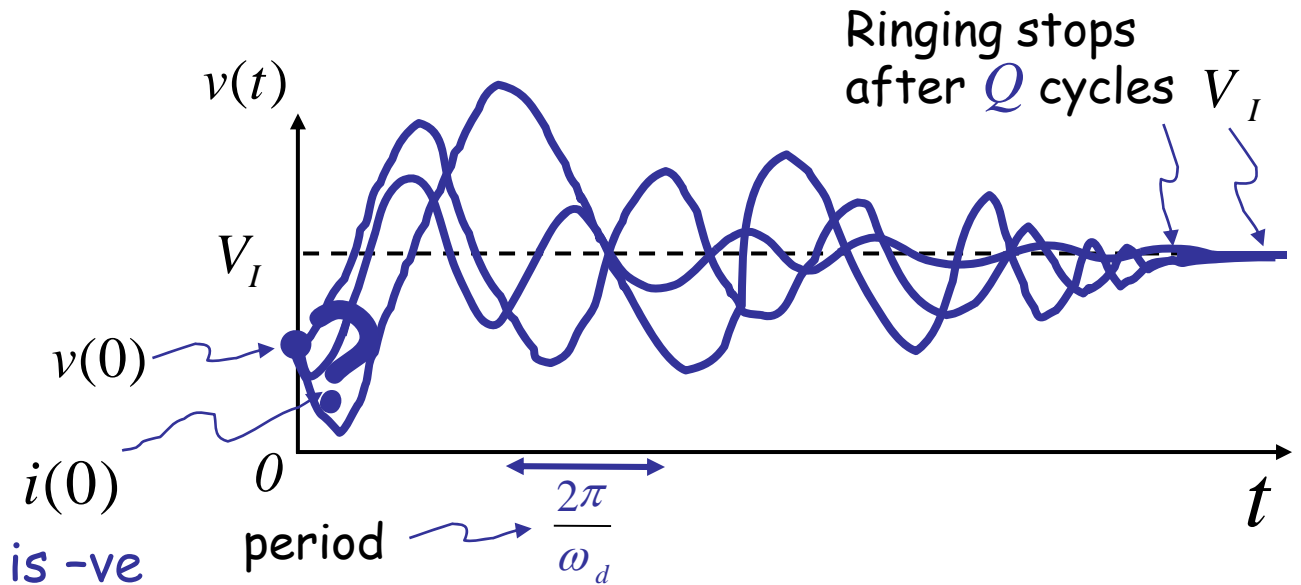

is -ve
so $v(t)$
must
drop


Characteristic
equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s^2 + 2\alpha s + \omega_o^2 = 0$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$Q = \frac{\omega_o}{2\alpha}$$

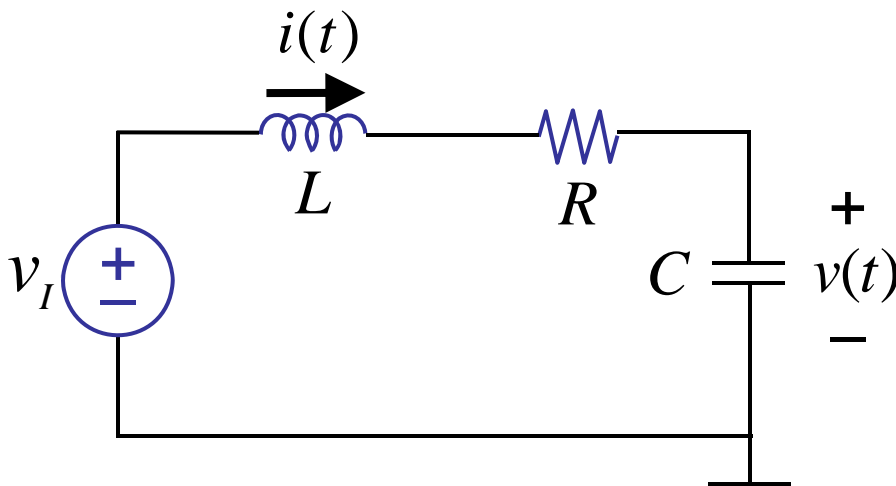

given
 $i(0)$ -ve
 $v(0)$ +ve