
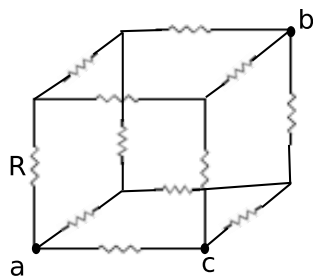


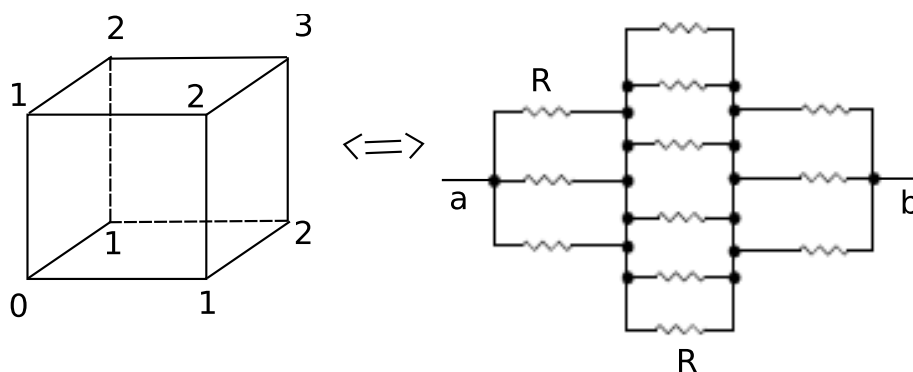8.022 Lecture Notes Class 32 - 11/14/2006



$$R_{eq} = \begin{cases} \frac{5}{6}R & a \rightarrow b \\ \frac{7}{12}R & a \rightarrow c \end{cases}$$

Same #'s have same potential, so dotted line wires have no current thru them.




Work to move charge :

$$dW = Vdq$$


Power :

$$P = \frac{dW}{dt} = V \frac{dq}{dt} = VI$$

$$P = VI = I^2R = \frac{V^2}{R}$$

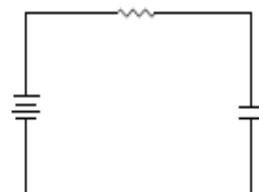


RC Circuits

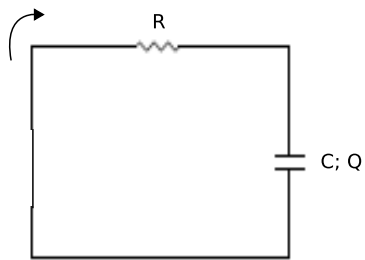

- Steady State is boring !

If capacitor is charged , $V = \frac{Q}{C}$ (voltage charge)

If not, $V = 0$ (like wire)

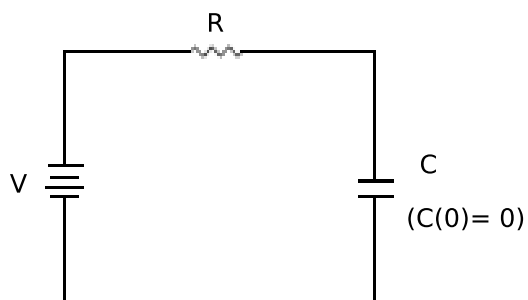

$$\Sigma \Delta V = \frac{Q}{C} - IR = 0 \quad I = -\frac{dQ}{dt}$$

$$\frac{Q}{C} + R \frac{dQ}{dt} = 0$$

Separate:

$$\int_{Q_0}^Q \frac{dQ}{Q} = \int_0^t -\frac{dt}{RC}$$


$$\ln \frac{Q}{Q_0} = -\frac{t}{RC}$$

$$Q = Q_0 e^{-\frac{t}{RC}} \quad \text{time constant } \tau = RC$$

$$I = -\frac{dQ}{dt}$$

$$= -Q_0 \cdot -\frac{1}{RC} e^{-\frac{t}{RC}}$$

$$= \frac{Q_0}{RC} e^{-\frac{t}{RC}}$$

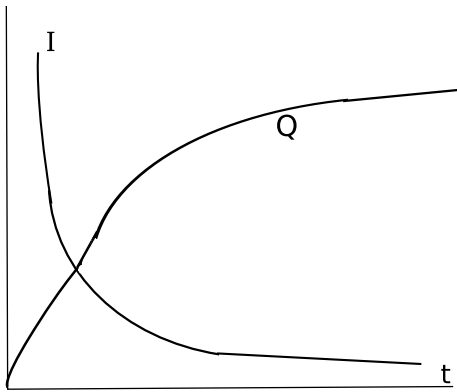

$$\begin{aligned}
V - \frac{Q}{C} - IR &= 0 \\
I &= -\frac{dQ}{dt} \\
V - \frac{Q}{C} &= R\frac{dQ}{dt} \\
\frac{d}{dt}\left(\frac{V - \frac{Q}{C}}{R}\right) &= CQ \\
\int_0^t \frac{dt}{RC} &= \int_0^Q \frac{dQ}{VC - Q} \\
\ln\left(\frac{CV - Q}{CV}\right) &= -\frac{t}{RC} \\
Q(t) &= CV(1 - e^{-\frac{t}{RC}}) \\
I(t) &= \frac{V}{R}e^{-\frac{t}{RC}}
\end{aligned}$$

- What about multiple V's and R's?

Thevenin's Theorem (Helmholtz)

Any combination of batteries and resistors with two terminals is equivalent to a battery and resistor in series

$$\text{from galvanometer} \begin{cases} \text{A - series (yes I) (low R)} \\ \text{V - parallel (no I) (high R)} \end{cases}$$