

Lecture 9 - MOSFET (I)

MOSFET I-V CHARACTERISTICS

October 6, 2005

Contents:

1. MOSFET: cross-section, layout, symbols
2. Qualitative operation
3. I-V characteristics

Reading assignment:


Howe and Sodini, Ch. 4, §§4.1-4.3

Announcements: Quiz 1: 10/13, 7:30-9:30 PM,
(lectures #1-9); open book; must have calculator.

Key questions

- How can carrier inversion be exploited to make a transistor?
- How does a MOSFET work?
- How does one construct a simple first-order model for the current-voltage characteristics of a MOSFET?

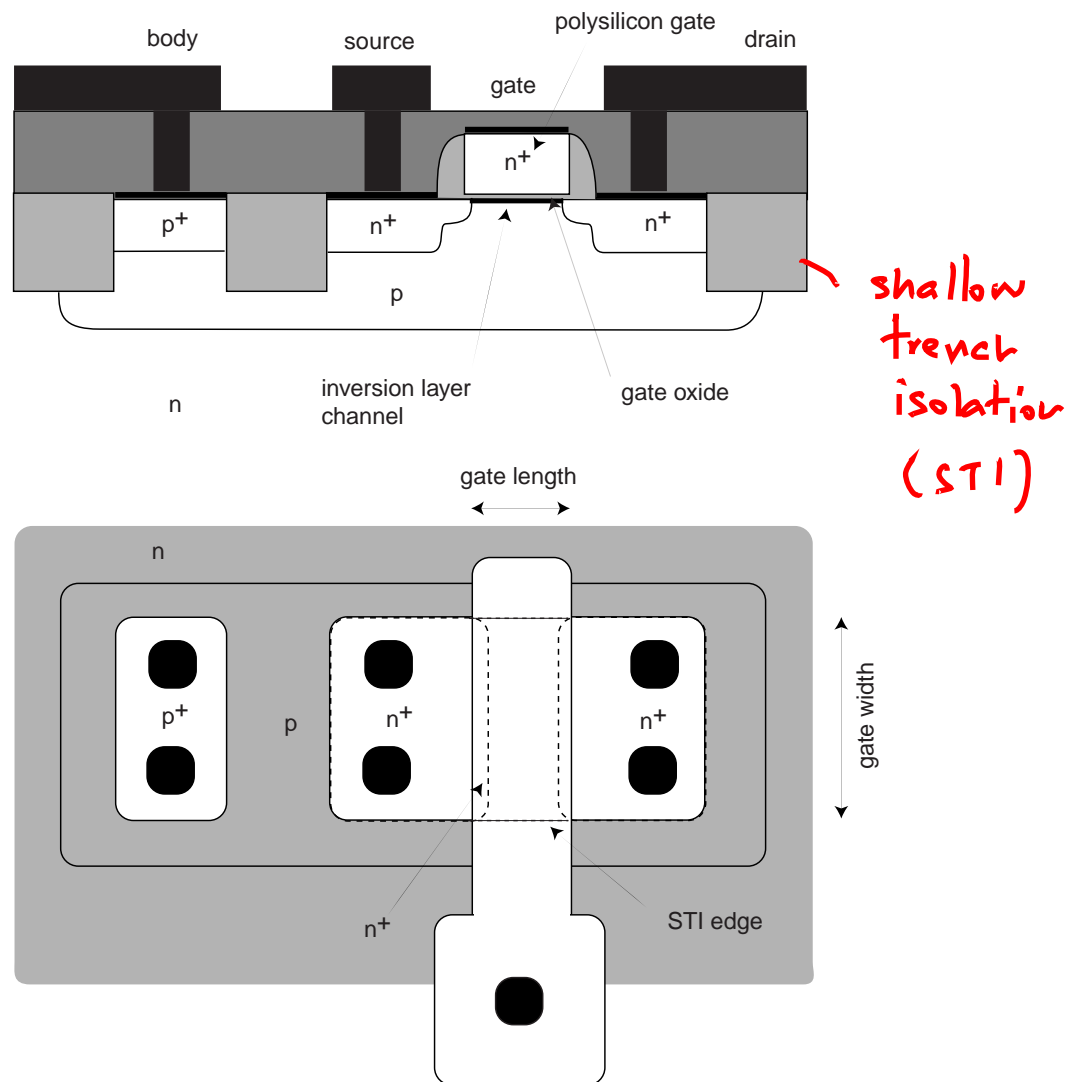1. MOSFET: layout, cross-section, symbols



Key elements:


- inversion layer under *gate* (depending on gate voltage)
- heavily-doped regions reach underneath gate \Rightarrow inversion layer electrically connects *source* and *drain*
- 4-terminal device: *body* voltage important

Image removed due to copyright restrictions.


□ Circuit symbols

Two complementary devices:


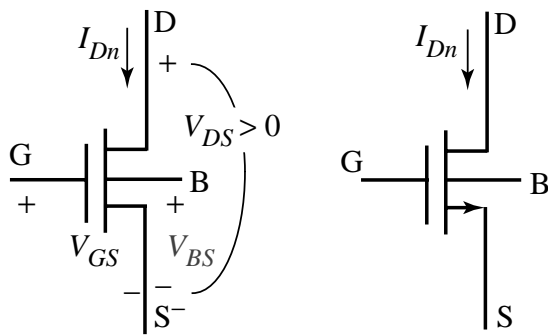
- n-channel device (n-MOSFET) on p-Si substrate
(uses electron inversion layer)
- p-channel device (p-MOSFET) on n-Si substrate
(uses hole inversion layer)



(a) n-channel MOSFET

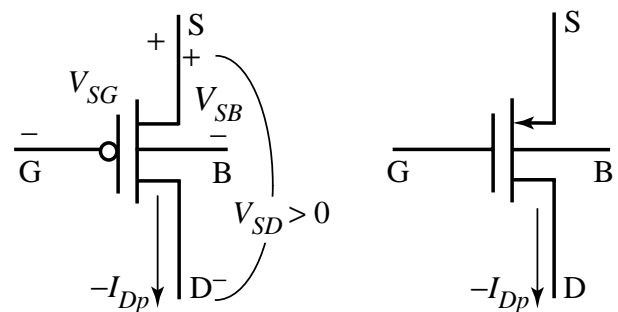


(b) p-channel MOSFET

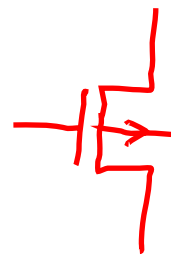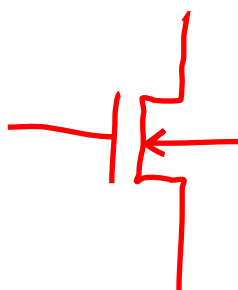

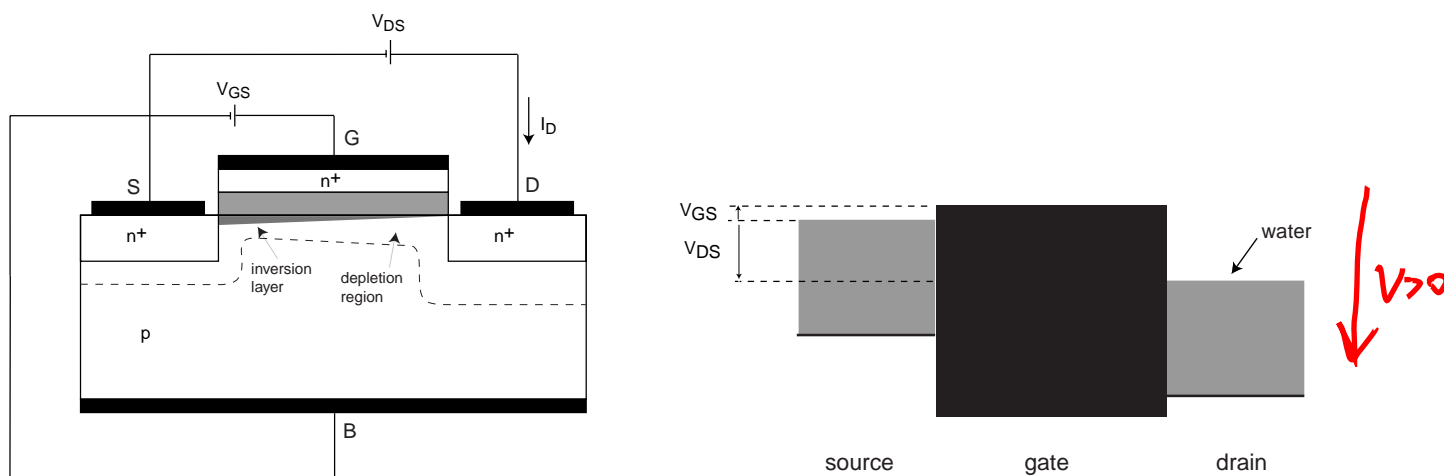2. Qualitative operation

Water analogy of MOSFET:

- *Source*: water reservoir
- *Drain*: water reservoir
- *Gate*: gate between source and drain reservoirs



Want to understand MOSFET operation as a function of:


- gate-to-source voltage (gate height over source water level)
- drain-to-source voltage (water level difference between reservoirs)

Initially consider source tied up to body (substrate or back).

Three regimes of operation:

□ **Cut-off regime:**

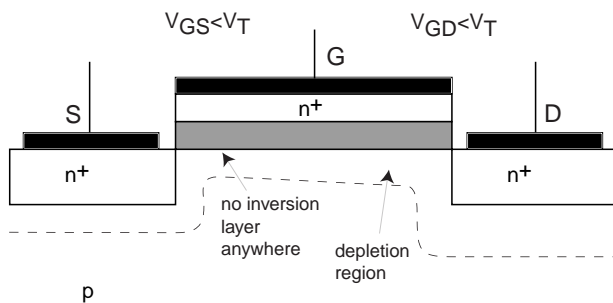
- MOSFET: $V_{GS} < V_T$, $V_{GD} < V_T$ with $V_{DS} > 0$.
- Water analogy: gate closed; no water can flow regardless of relative height of source and drain reservoirs.



$$I_D = 0$$



□ **Linear or Triode regime:**

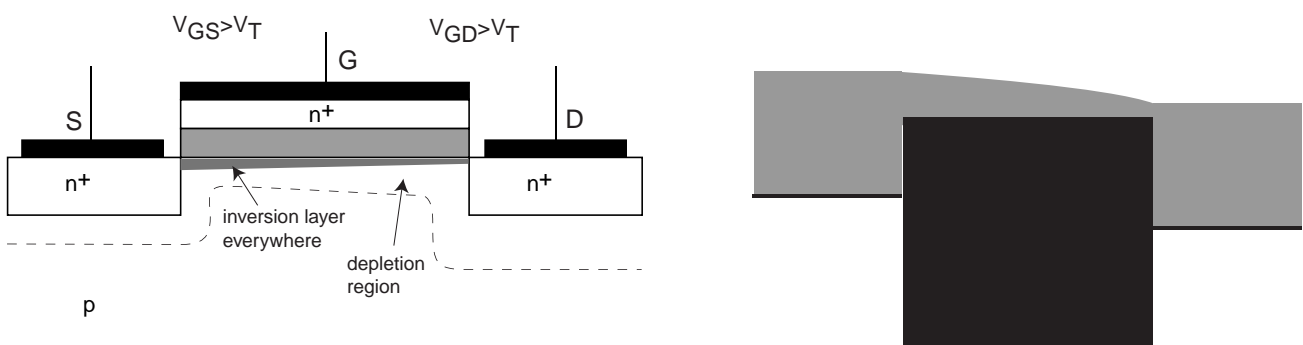- MOSFET: $V_{GS} > V_T$, $V_{GD} > V_T$, with $V_{DS} > 0$.
- Water analogy: gate open but small difference in height between source and drain; water flows.




Electrons drift from source to drain \Rightarrow electrical current!

- $V_{GS} \uparrow \rightarrow |Q_n| \uparrow \rightarrow I_D \uparrow$
- $V_{DS} \uparrow \rightarrow |E_y| \uparrow \rightarrow I_D \uparrow$

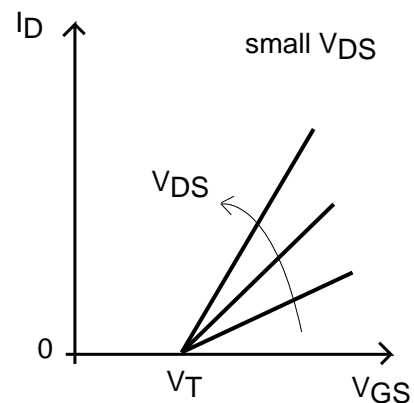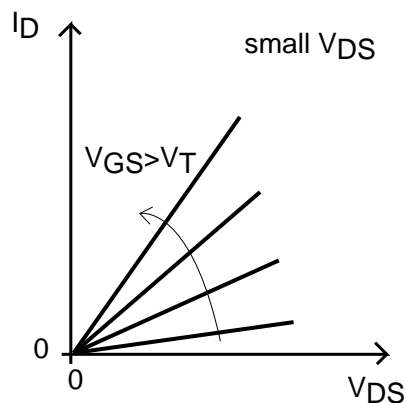


□ **Saturation regime:**

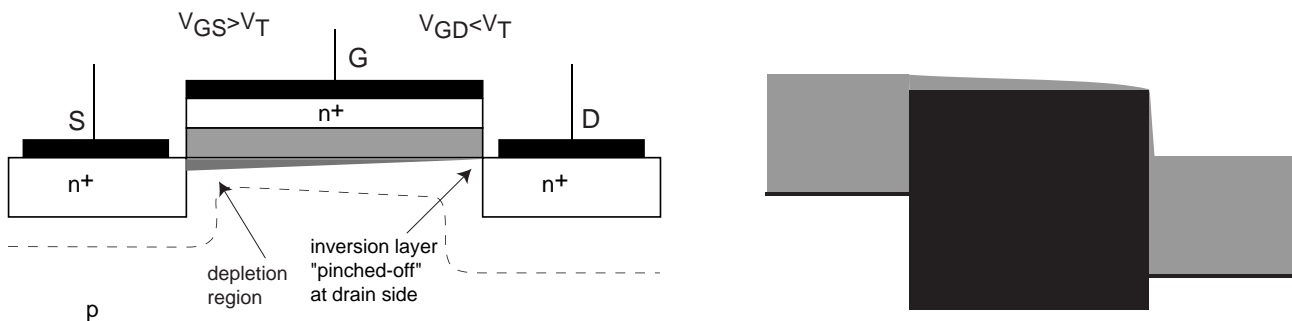- MOSFET: $V_{GS} > V_T$, $V_{GD} < V_T$ ($V_{DS} > 0$).
- Water analogy: gate open; water flows from source to drain, but free-drop on drain side \Rightarrow total flow independent of relative reservoir height!




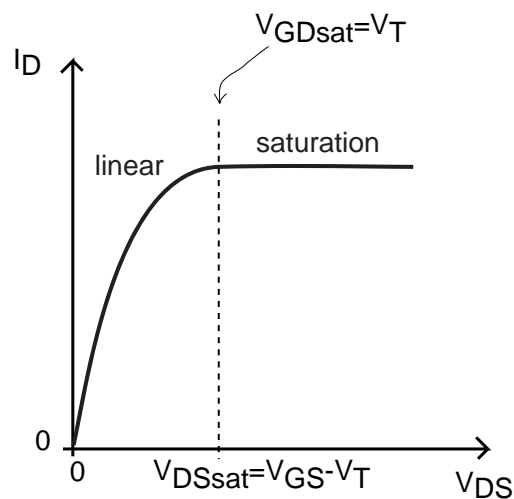I_D independent of V_{DS} : $I_D = I_{Dsat}$



3. I-V characteristics

Geometry of problem:

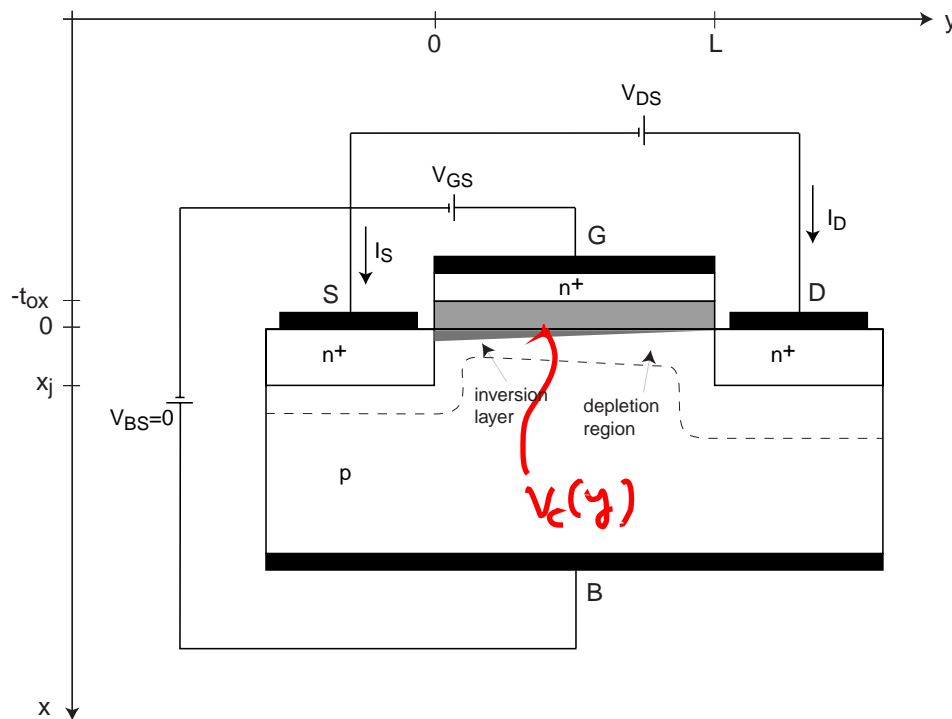

□ General expression of channel current

Current can only flow in y -direction:

independent of y →

$$I_y = W Q_n(y) v_y(y)$$

W → cm
 Q_n → C/cm^2
 v_y → cm/s

$Q_n < 0$
 $v_y < 0$

Drain terminal current is equal to *minus* channel current:

$$I_D = -W Q_n(y) v_y(y) **$$

$$I_D = -WQ_n(y)v_y(y)$$

Rewrite in terms of voltage at channel location y , $V_c(y)$:

- If electric field is not too big:

$$v_y(y) \simeq -\mu_n E_y(y) = \mu_n \frac{dV_c(y)}{dy}$$

- For $Q_n(y)$ use charge-control relation at location y :

$$Q_n(y) = -C_{ox} [\underbrace{V_{GS} - V_c(y)}_{\text{gate-channel voltage}} - V_T]$$

local channel voltage
"overdrive"

for $V_{GS} - V_c(y) \geq V_T$.

gate-channel
voltage

All together:

$$I_D = W \mu_n C_{ox} (V_{GS} - V_c(y) - V_T) \frac{dV_c(y)}{dy}$$

Simple linear first-order differential equation with one unknown, the channel voltage $V_c(y)$.

Solve by separating variables:

$$I_D dy = W \mu_n C_{ox} (V_{GS} - V_c - V_T) dV_c$$

Integrate along the channel in the linear regime:

source
end \rightarrow for $y = 0$, $V_c(0) = 0$

drain
end \rightarrow for $y = L$, $V_c(L) = V_{DS}$ (linear regime)

Then:

$$I_D \int_0^L dy = W \mu_n C_{ox} \int_0^{V_{DS}} (V_{GS} - V_c - V_T) dV_c$$

or:

$$I_D = \frac{W}{L} \mu_n C_{ox} \left(V_{GS} - \frac{V_{DS}}{2} - V_T \right) V_{DS}$$



*

For small V_{DS} :

$$I_D \simeq \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_T) V_{DS}$$

Key dependencies:

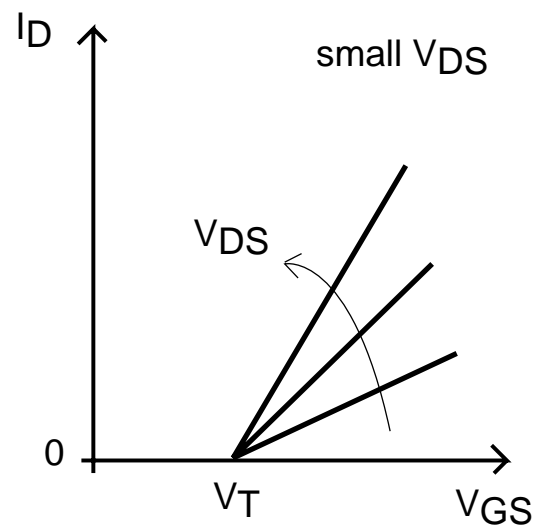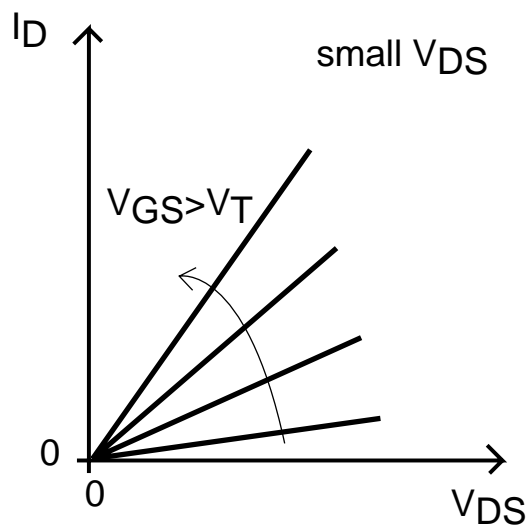- $V_{DS} \uparrow \rightarrow I_D \uparrow$ (higher lateral electric field)
- $V_{GS} \uparrow \rightarrow I_D \uparrow$ (higher electron concentration)
- $L \uparrow \rightarrow I_D \downarrow$ (lower lateral electric field)
- $W \uparrow \rightarrow I_D \uparrow$ (wider conduction channel)



This is the linear or triode regime.

In general,


$$I_D = \frac{W}{L} \mu_n C_{ox} (V_{GS} - \frac{V_{DS}}{2} - V_T) V_{DS}$$

Equation valid if $V_{GS} - V_c(y) \geq V_T$ at every y .

Worst point is $y = L$, where $V_c(y) = V_{DS}$, hence, equation valid if $V_{GS} - V_{DS} \geq V_T$, or:

$$V_{DS} \leq V_{GS} - V_T$$


locus of
linear regime
with $V_{DS} > 0$

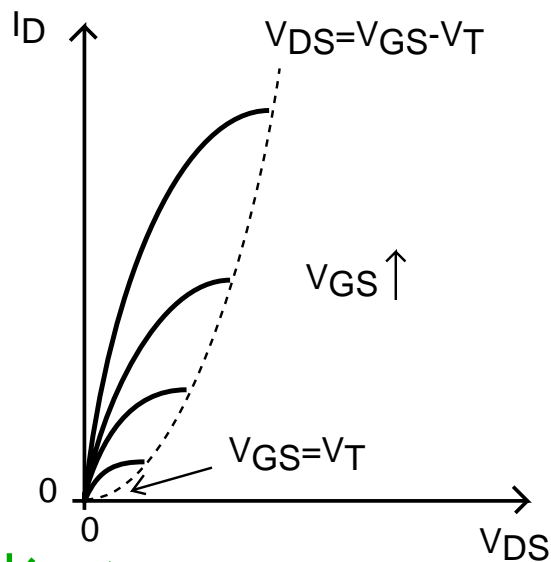

Note: $\frac{dI_D}{dV_{DS}} \rightarrow 0$ as $V_{DS} \rightarrow V_{GS} - V_T$

term responsible for bend over of I_D : $-\frac{V_{DS}}{2}$

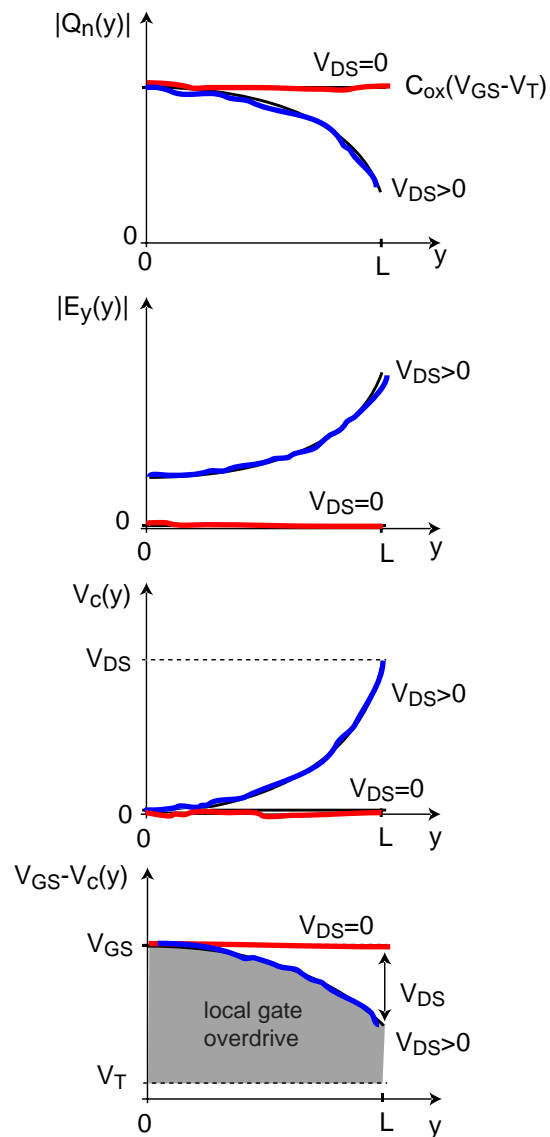To understand why I_D bends over, must understand first **channel debiasing**:




Along channel from source to drain:

$$y \uparrow \rightarrow V_c(y) \uparrow \rightarrow |Q_n(y)| \downarrow \rightarrow |E_y(y)| \uparrow$$

Local "channel overdrive" reduced closer to drain.


Impact of V_{DS} :

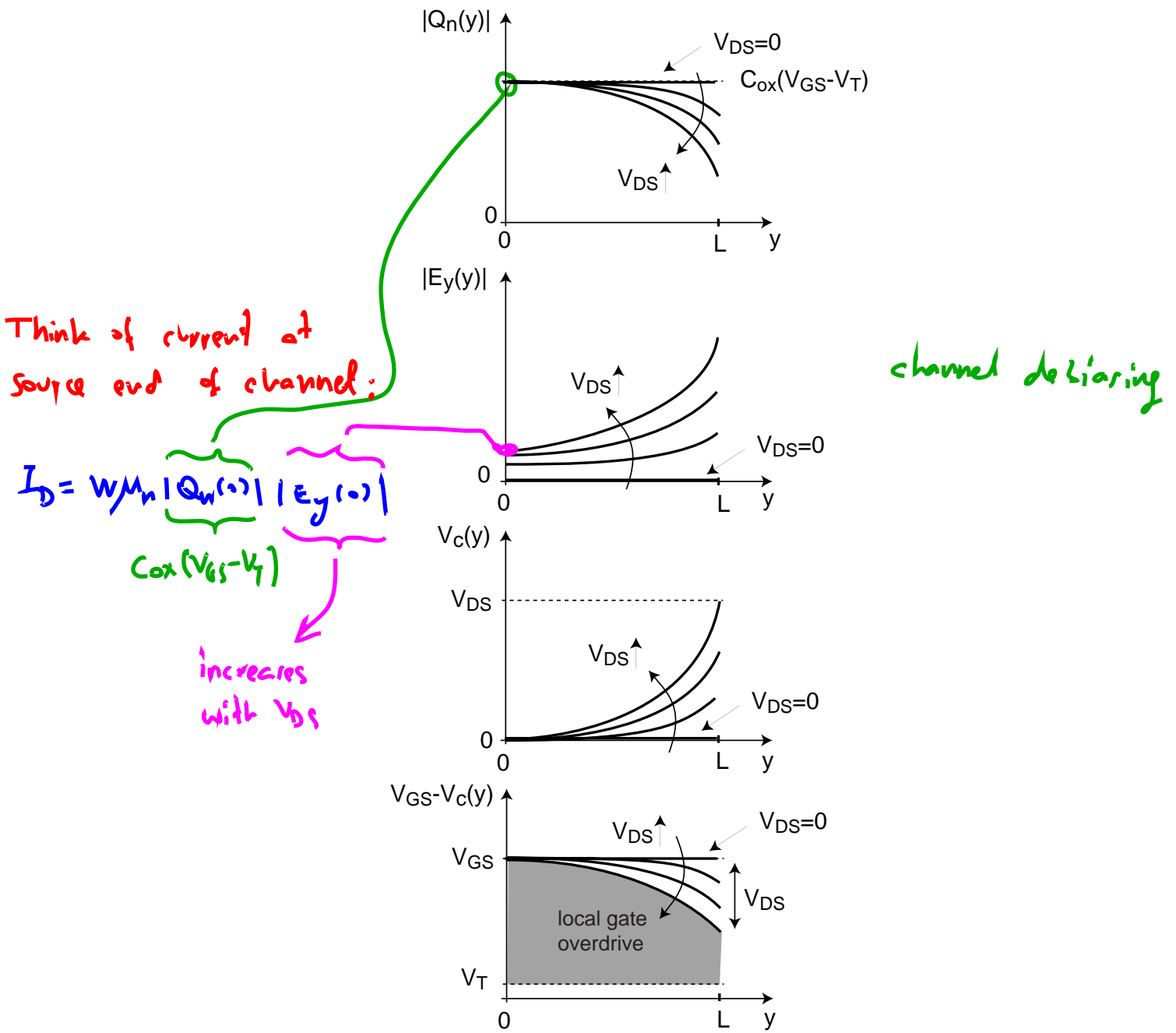


As $V_{DS} \uparrow$, channel debiasing more prominent
 $\Rightarrow I_D$ rises more slowly with V_{DS}

$3\mu\text{m}$ n-channel MOSFET

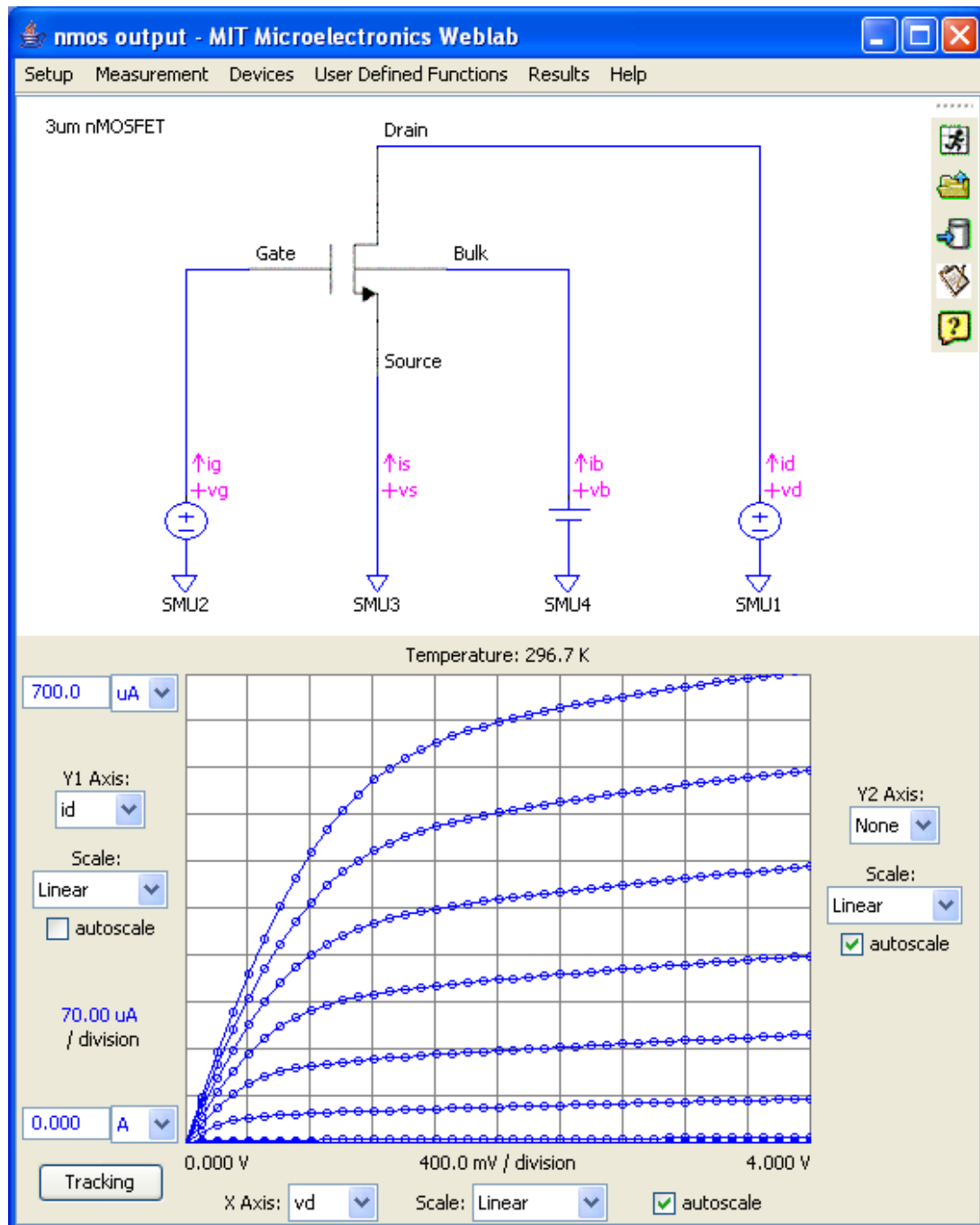
Output characteristics ($V_{GS} = 0 - 4\text{ V}$, $\Delta V_{GS} = 0.5\text{ V}$):



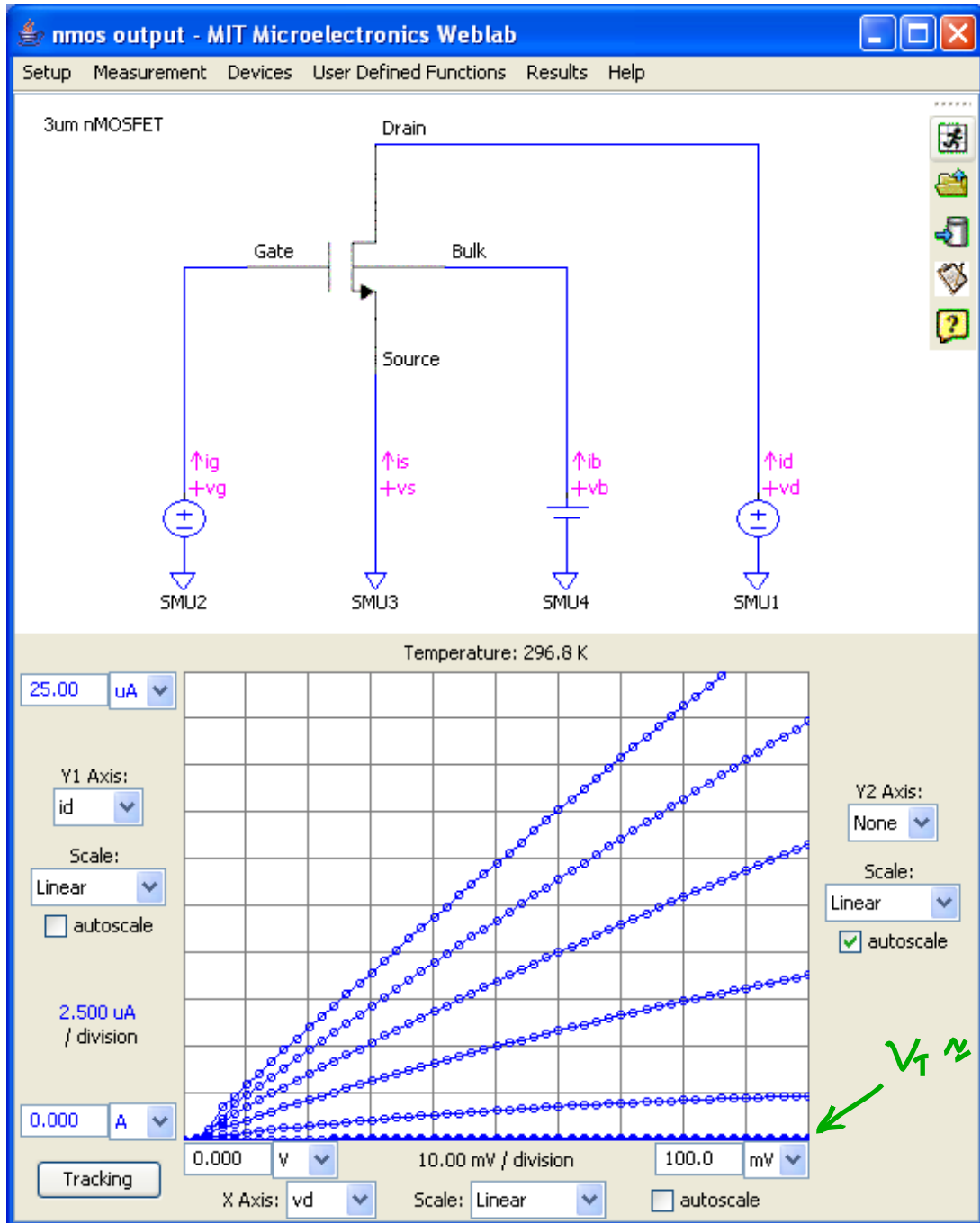Zoom close to origin ($V_{GS} = 0 - 2 V, \Delta V_{GS} = 0.25 V$):



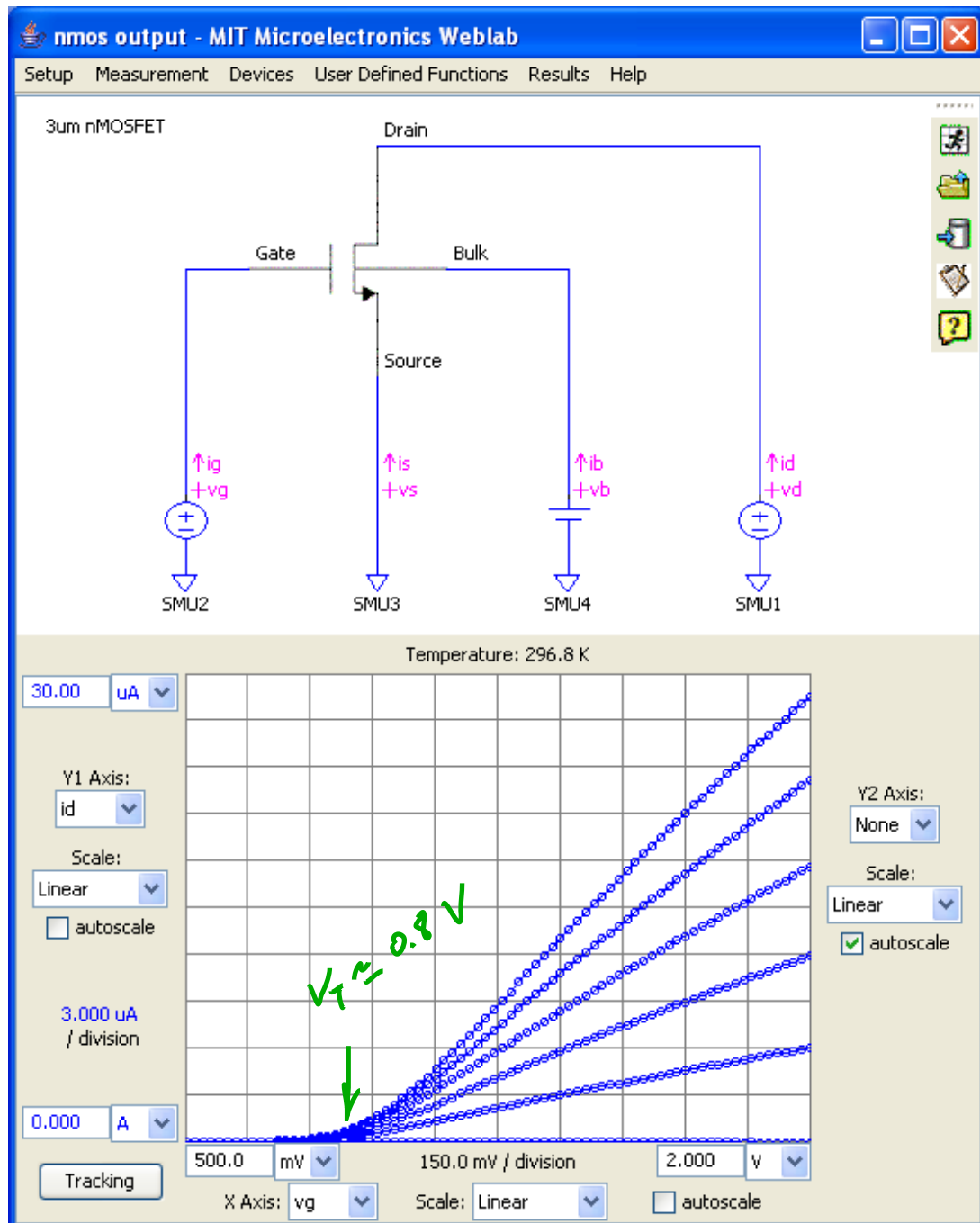Transfer characteristics ($V_{DS} = 0 - 100 \text{ mV}$, $\Delta V_{DS} = 20 \text{ mV}$):



Key conclusions

- The MOSFET is a *field-effect transistor*:
 - the amount of charge in the inversion layer is controlled by the field-effect action of the gate
 - the charge in the inversion layer is mobile \Rightarrow conduction possible between source and drain
- In the *linear regime*:
 - $V_{GS} \uparrow \Rightarrow I_D \uparrow$: more electrons in the channel
 - $V_{DS} \uparrow \Rightarrow I_D \uparrow$: stronger field pulling electrons out of the source
- *Channel debiasing*: inversion layer "thins down" from source to drain \Rightarrow current saturation as V_{DS} approaches:

$$V_{DSsat} = V_{GS} - V_T$$